
System I

Computational Operations & Units

Haifeng Liu

Zhejiang University

Overview

- Addition
- Subtraction
- Arithmetic logic unit (ALU)
- Multiplication
- Division
- Floating number operations

Overview

- Addition
- Subtraction
- Arithmetic logic unit (ALU)
- Multiplication
- Division
- Floating number operations

Iterative Combinational Circuits

- Arithmetic functions
 - Operate on binary vectors
 - Use the same subfunction in each bit position
- Can design functional block for subfunction and repeat to obtain functional block for overall function
- *Cell* - subfunction block
- *Iterative array* - a array of interconnected cells
- An iterative array can be in a single dimension (1D) or multiple dimensions


1-bit adder: Half-Adder

- A 2-input, 1-bit width binary adder that performs the following computations:

A	0	0	1	1
+ B	+ 0	+ 1	+ 0	+ 1
C F	0 0	0 1	0 1	1 0

- A half adder adds two bits to produce a two-bit sum
- The sum is expressed as a sum bit , F and a carry bit, C
- The half adder can be specified as a truth table for F and C \Rightarrow

A	B	F	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

1-bit adder: Full Adder

- A full adder is similar to a half adder, but includes a carry-in bit from lower stages.
- Like the half-adder, it computes a sum bit **F** and a carry bit

C_{in}

- For a carry-in (**C_{in}**) of 0, it is the same as the half-adder:


C_{in}	0	0	0	0
A	0	0	1	1
+ B	+ 0	+ 1	+ 0	+ 1
C_{out} F	0 0	0 1	0 1	1 0

- For a carry-in (**C_{in}**) of 1:


C_{in}	1	1	1	1
A	0	0	1	1
+ B	+ 0	+ 1	+ 0	+ 1
C_{out} F	0 1	1 0	1 0	1 1

Classic Designs: Full Adder (cont'd)

Input			Output	
A	B	C_{in}	F	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Classic Designs: Full Adder (cont'd)

 

Multibit Carry Propagate Adders (CPA)

- Types of CPA

 
- Ripple-carry (slow)
- Carry Skip
- Carry Select
- Carry-lookahead (fast)
- Prefix (fast)



- Faster adders require more hardware

Ripple-Carry Adder (RCA)

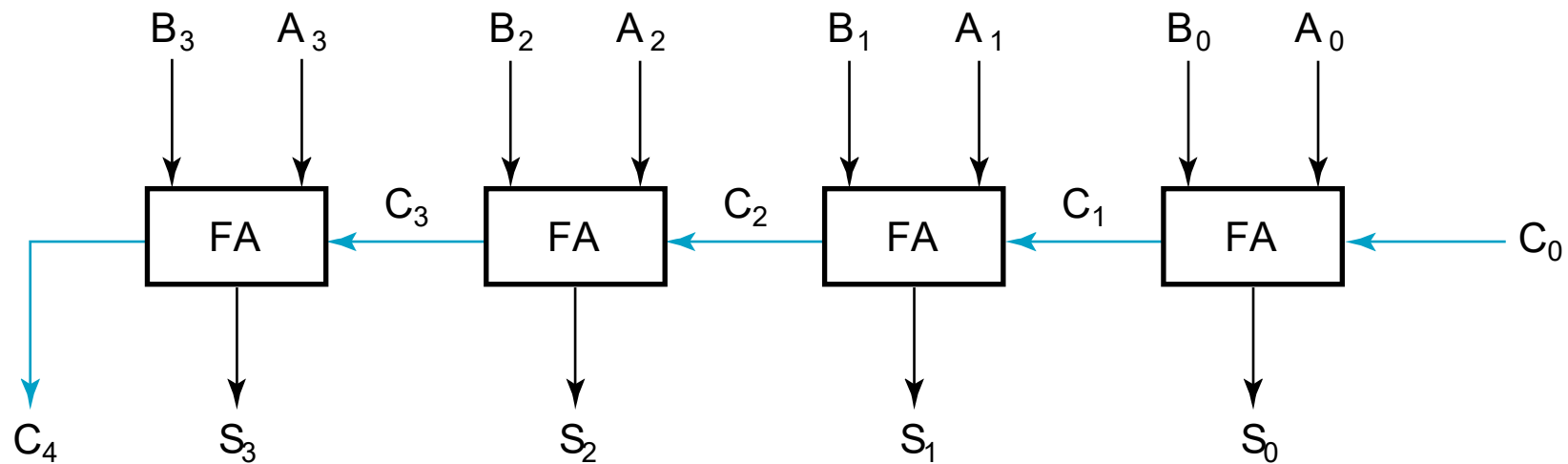- Chain 1-bit adders together
- Carry ripples through entire chain
- Disadvantage: **slow**



Ripple-Carry Adder Delay

$$t_{ripple} = Nt_{FA}$$

t_{FA} : delay of a 1-bit full adder

Carry Lookahead Adder


$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

 - For a given i-bit binary adder,
 - If $A_i = B_i = \text{"1"}$ and whatever C_i is, we have carry out as 1, that is $C_{i+1} = 1$
 - If the output of half adder is 1 and we have carry in as 1, we have carry out as 1, that is $C_{i+1} = 1$
- These two conditions of setting carry out as 1 is called *generate* (G_i) and *propagate* (P_i).



Carry Lookahead Development

- $C_{i+1} = G_i + P_i C_i$ can be removed from the cells and used to derive a set of carry equations spanning multiple cells.

- Beginning at the cell 0 with carry in C_0 :


$$C_1 = G_0 + P_0 C_0$$

$$\begin{aligned} C_2 &= G_1 + P_1 C_1 = G_1 + P_1(G_0 + P_0 C_0) \\ &= G_1 + P_1 G_0 + P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_3 &= G_2 + P_2 C_2 = G_2 + P_2(G_1 + P_1 G_0 + P_1 P_0 C_0) \\ &= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \end{aligned}$$

$$\begin{aligned} C_4 &= G_3 + P_3 C_3 \\ &= G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \end{aligned}$$

4-Bit CLA

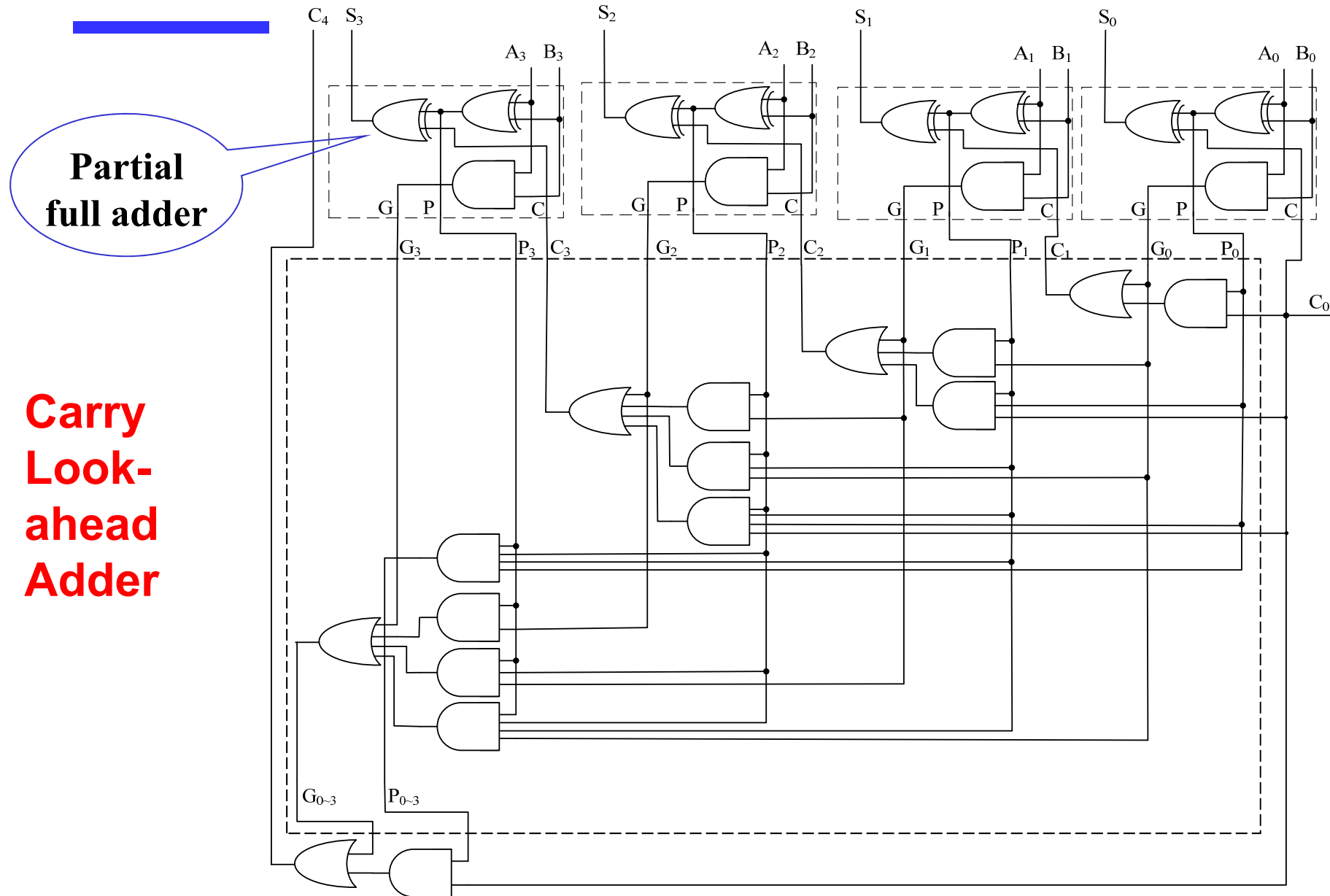

Group Carry Lookahead Logic

- Figure in the previous slide shows the implementation of these equations for four bits. This could be extended to more than four bits; in practice, due to limited gate fan-in, such extension is not feasible.
- $C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$
- Instead, the concept is extended another level by considering *group generate* (G_{0-3}) and *group propagate* (P_{0-3}) functions:

$$G_{0-3} = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 P_0 G_0$$
$$P_{0-3} = P_3 P_2 P_1 P_0$$

- Using these two equations:

$$C_4 = G_{0-3} + P_{0-3} C_0$$

- Thus, it is possible to have four 4-bit adders use one of the same carry lookahead circuit to speed up 16-bit addition

Group Carry Lookahead Logic (Cont.)

- $C_4 = G_3 + P_3G_2 + P_3P_2G_1 + P_3P_2P_1G_0 + P_3P_2P_1P_0C_0 = G_{0\sim3} + P_{0\sim3}C_0$
- $C_8 = G_7 + P_7G_6 + P_7P_6G_5 + P_7P_6P_5G_4 + P_7P_6P_5P_4C_4 = G_{4\sim7} + P_{4\sim7}C_4$
- $C_{12} = G_{11} + P_{11}G_{10} + P_{11}P_{10}G_9 + P_{11}P_{10}P_9G_8 + P_{11}P_{10}P_9P_8C_8 = G_{8\sim11} + P_{8\sim11}C_8$
- $C_{16} = G_{15} + P_{15}G_{14} + P_{15}P_{14}G_{13} + P_{15}P_{14}P_{13}G_{12} + P_{15}P_{14}P_{13}P_{12}C_{12} = G_{12\sim15} + P_{12\sim15}C_{12}$

Group Carry Lookahead Logic (Cont.)

- $C_4 = G_{0\sim3} + P_{0\sim3}C_0$
- $C_8 = G_{4\sim7} + P_{4\sim7}C_4$
- $C_{12} = G_{8\sim11} + P_{8\sim11}C_8$
- $C_{16} = G_{12\sim15} + P_{12\sim15}C_{12}$

$$C_1 = G_0 + P_0 C_0$$

$$C_2 = G_1 + P_1 C_1$$

$$C_3 = G_2 + P_2 C_2$$

$$C_4 = G_3 + P_3 C_3$$


Carry Lookahead Example

- Specifications:

- 16-bit CLA

- Delays:

 - NOT = 1
- XOR = Isolated AND = 3
- AND-OR = 2




- Longest Delays:

- Ripple carry adder* = $3 + 15 \times 2 + 3 = 36$
- CLA = $3 + 3 \times 2 + 3 = 12$

Carry skip adder

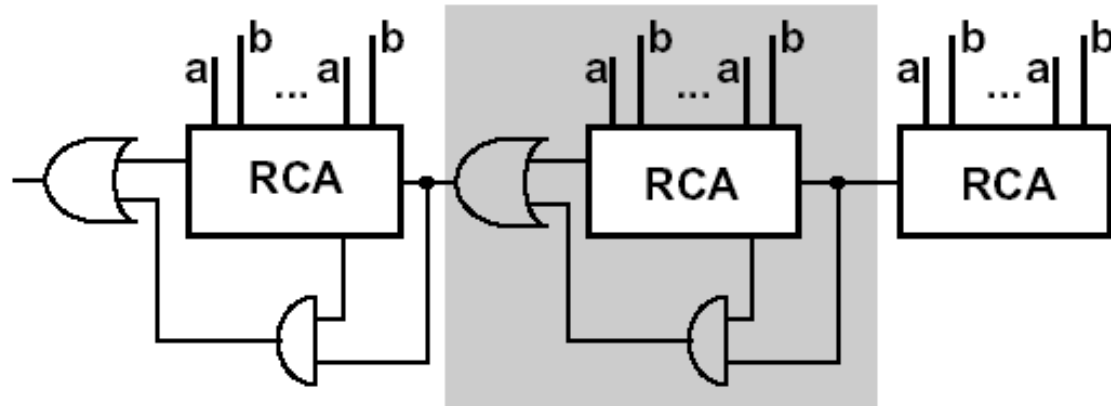- Accelerating the carry by skipping the interior blocks
- Optimal speed with no-equal distribution of block length



Carry skip adder


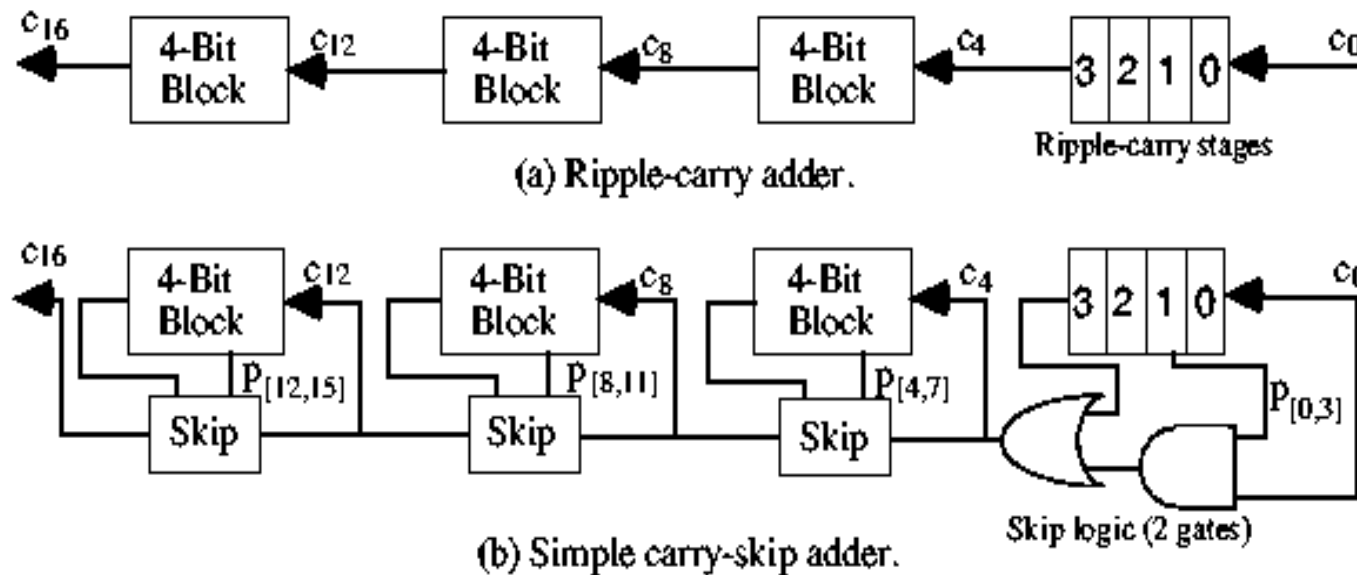



Fig. 7.1 Converting a 16-bit ripple-carry adder into a simple carry-skip adder with 4-bit skip blocks.

Carry select adder (CSA)

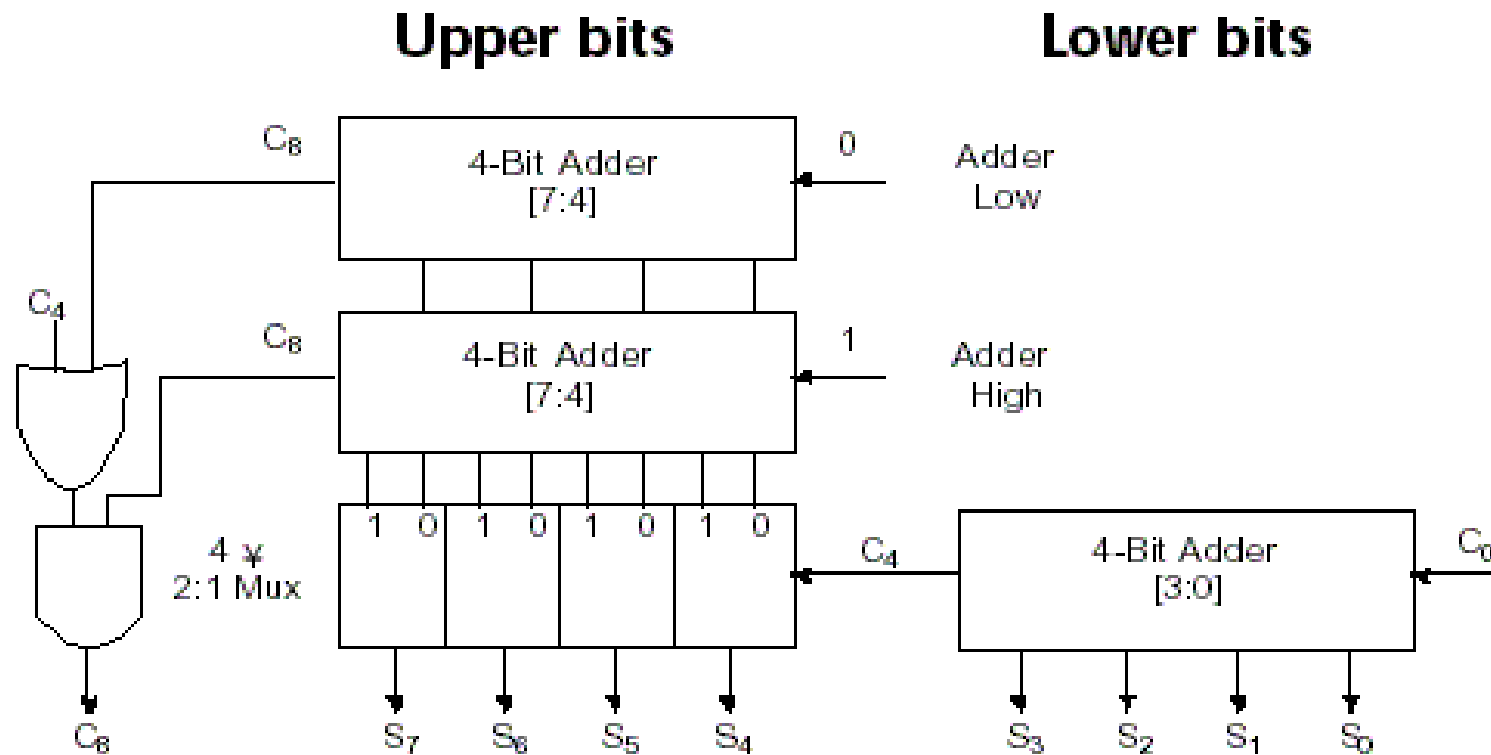

Carry select adder

- Carry selection by nibbles

 

Prefix Adder

- Computes carry in (C_{i-1}) for each column, then computes sum:

$$S_i = (A_i \oplus B_i) \oplus C_{i-1}$$

- Computes G and P for 1-, 2-, 4-, 8-bit blocks, etc. until all G_i (carry in) known
- $\log_2 N$ stages

Prefix Adder (cont'd)

- Carry in either *generated* in a column or *propagated* from a previous column.

- Column -1 holds C_{in} , so

$$G_{-1} = C_{in}, P_{-1} = 0$$

- Carry in to column i == carry out of column $i-1$:

$$C_{i-1} = G_{i-1:-1}$$

$G_{i-1:-1}$: generate signal spanning columns $i-1$ to -1

- Sum equation:

$$S_i = (A_i \oplus B_i) \oplus G_{i-1:-1}$$

- **Goal:** Quickly compute $G_{0:-1}, G_{1:-1}, G_{2:-1}, G_{3:-1}, G_{4:-1}, G_{5:-1}, \dots$
(called *prefixes*)




Prefix Adder (cont'd)

- Generate and propagate signals for a block spanning bits $i:j$:


$$G_{i:j} = G_{i:k} + P_{i:k} G_{k-1:j}$$

$$P_{i:j} = P_{i:k} P_{k-1:j}$$

 
 
 
- In words:
 - **Generate:** block $i:j$ will generate a carry if:
 - upper part ($i:k$) generates a carry or
 - upper part propagates a carry generated in lower part ($k-1:j$)
 - **Propagate:** block $i:j$ will propagate a carry if *both* the upper and lower parts propagate the carry



Prefix Adder Schematic

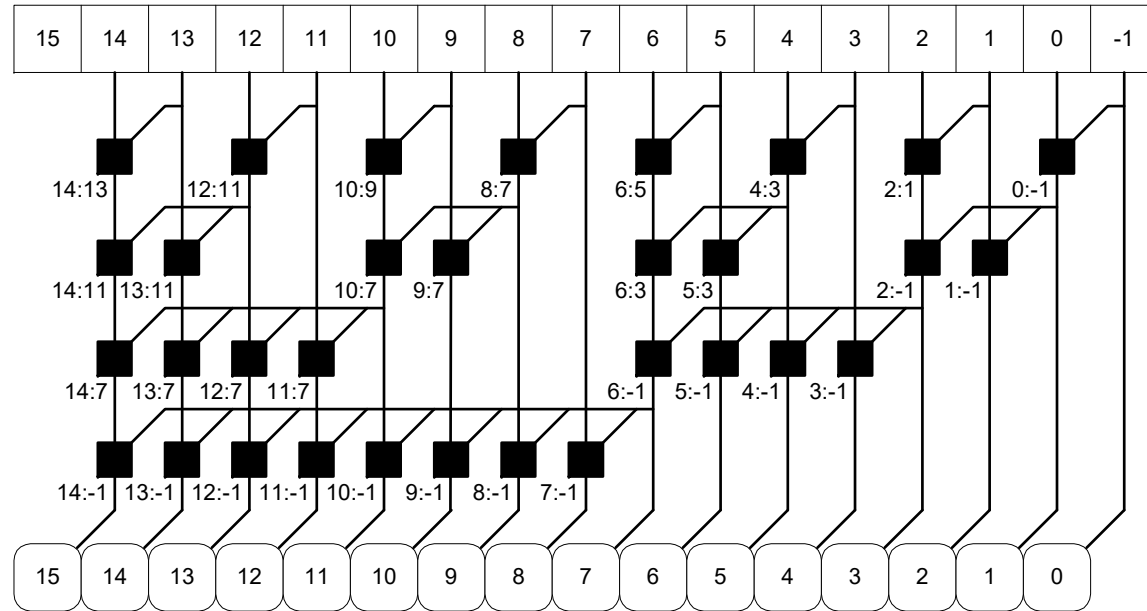

Legend

   

Prefix Adder Delay

$$t_{PA} = t_{pg} + \log_2 N(t_{pg_prefix}) + t_{XOR}$$

t_{pg} : delay to produce P_iG_i (AND or OR gate)

t_{pg_prefix} : delay of black prefix cell (AND-OR gate)

Overview

- Addition
- Subtraction
- Arithmetic logic unit (ALU)
- Multiplication
- Division
- Floating number operations

Unsigned Subtraction

- For n-digit, unsigned numbers M and N, find $M - N$ in base 2:
 - Add the 2's complement of the subtrahend N to the minuend M:
$$M + (2^n - N) = M - N + 2^n$$
 - If $M \geq N$, the sum produces end carry r^n which is discarded; from above, $M - N$ remains.
 - If $M < N$, the sum does not produce an end carry and, from above, is equal to $2^n - (N - M)$, the 2's complement of $(N - M)$.
 - To obtain the result $-(N - M)$, take the 2's complement of the sum and place a $-$ to its left.

Unsigned 2's Complement Subtraction

Example 1

- Find $01010100_2 - 01000011_2$

$$\begin{array}{r} 01010100 \\ - 01000011 \end{array} \xrightarrow{\text{2's comp}} \begin{array}{r} 1\ 01010100 \\ + 10111101 \\ \hline 00010001 \end{array}$$

- The carry of 1 indicates that no correction of the result is required.

Unsigned 2's Complement Subtraction

Example 2

- Find $01000011_2 - 01010100_2$

$$\begin{array}{r}
 01000011 \\
 - 01010100 \\
 \hline
 \end{array}
 \xrightarrow{\text{2's comp}}
 \begin{array}{r}
 0 \quad 01000011 \\
 + 10101100 \\
 \hline
 11101111 \\
 \xrightarrow{\text{2's comp}} \\
 00010001
 \end{array}$$

- The carry of 0 indicates that a correction of the result is required.
- Result = $-(00010001)$

Signed 2's Complement Arithmetic Examples


- Signed binary addition using 2s complement

+ 6	00000110	- 6	11111010	+ 6	00000110	- 6	11111010
+ 13	<u>00001101</u>	+ 13	<u>00001101</u>	- 13	<u>11110011</u>	- 13	<u>11110011</u>
+ 19	00010011	+ 7	00000111	- 7	11111001	- 19	11101101

- Signed binary subtraction using 2s complement

- 6	11111010	11111010	+ 6	00000110	00000110
- (-13)	- 11110011	+ 00001101	- (-13)	- 11110011	+ 00001101
<u> </u>	<u> </u>	<u> </u>	<u> </u>	<u> </u>	<u> </u>
+ 7		00000111	+ 19		00010011

4-Bit Binary Adder-Subtractors


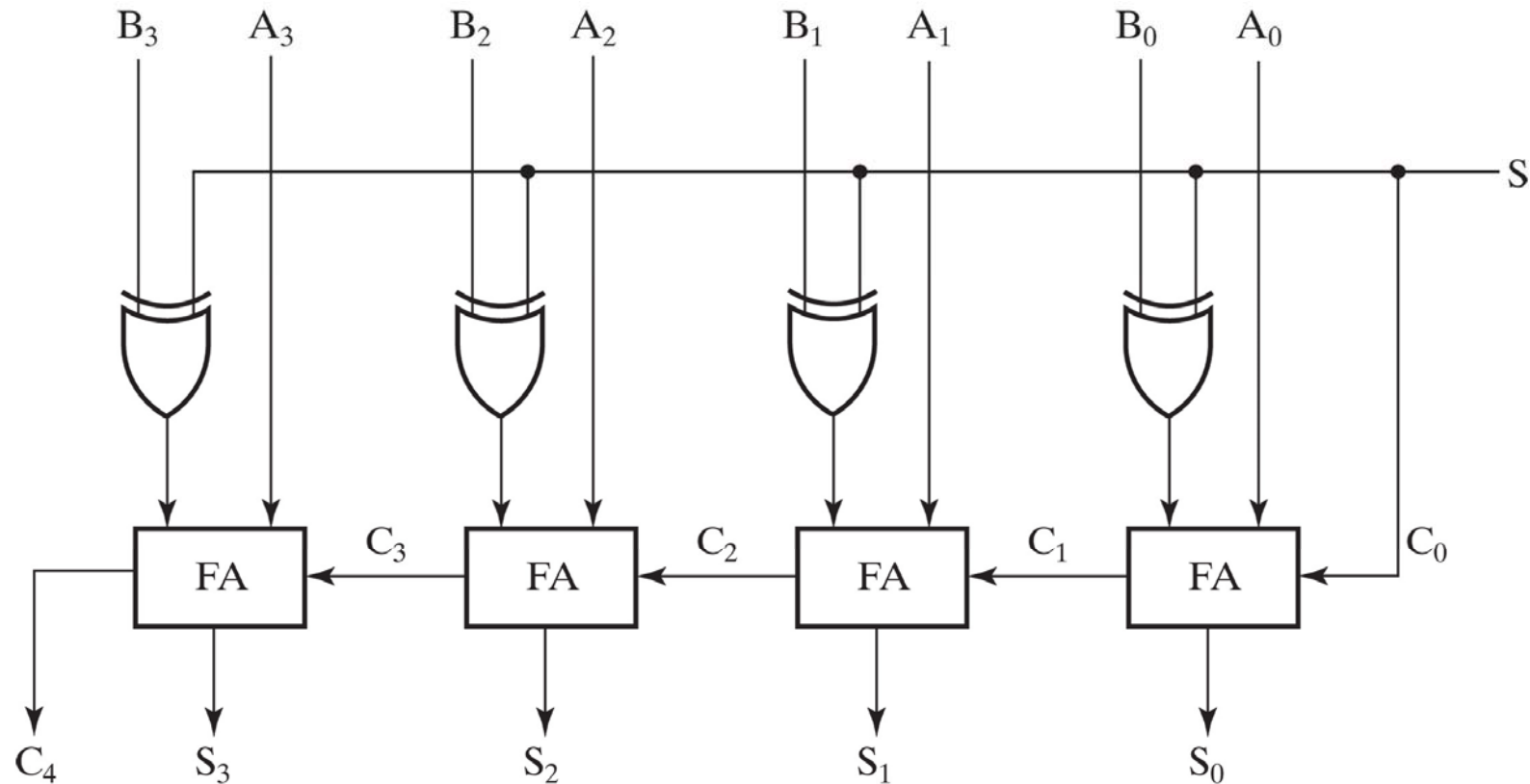


Copyright ©2016 Pearson Education, All Rights Reserved

- When $S=0$: Addition ($A+B$)
- When $S=1$: Subtraction ($A+2$'s complement of B)
- Can be used to add/subtract unsigned numbers and signed 2's complement numbers

Addition/Subtraction

  - Both can be handled by using 2's complement representation
- Can achieve a unified implementation
 - Addition vs. subtraction
 - Unsigned vs. signed



- Corner cases shall be considered
 - Some important flags

Carry & Overflow

- Carry is important when...
 - Adding or subtracting *unsigned integers*
 - Indicates that the unsigned sum is out of range
 - Either < 0 or $>$ maximum unsigned n-bit value
- Overflow is important when...
 - Adding or subtracting *signed integers*
 - Indicates that the signed sum is out of range
- Overflow occurs when?

Signed Overflow

- With two's complement and a 4-bit adder, for example, the largest representable decimal number is +7, and the smallest is -8.

- What if you try to compute $4 + 5$, or $(-4) + (-5)$?

$$\begin{array}{r} 0100 \quad (+4) \\ + 0101 \quad (+5) \\ \hline 01001 \quad (-7) \end{array}$$

$$\begin{array}{r} 1100 \quad (-4) \\ + 1011 \quad (-5) \\ \hline 10111 \quad (+7) \end{array}$$

- We cannot just include the carry out to produce a five-digit result, as for unsigned addition. If we did, $(-4) + (-5)$ would result in +23!
- Also, unlike the case with unsigned numbers, the carry out cannot be used to detect overflow, by itself
 - In the example on the left, the carry out is 0 but there is overflow.
 - Conversely, there are situations where the carry out is 1 but there is no overflow.

How to Detect Signed Overflow?

- The impact of carry and overflow

Expression	Result	Carry?	Overflow?	Correct Result?
0100 (+4) + 0010 (+2)	0110 (+6)	No	No	Yes
0100 (+4) + 0110 (+6)	1010 (-6)	No	Yes	No
1100 (-4) + 1110 (-2)	1010 (-6)	Yes	No	Yes
1100 (-4) + 1010 (-6)	0110 (+6)	Yes	Yes	No

Examples of four *signed* additions

- The easiest way to detect signed overflow is to look at all the sign bits.

$$\begin{array}{r}
 \textcircled{0}100 \quad (+4) \\
 + \textcircled{0}101 \quad (+5) \\
 \hline
 0\textcircled{1}001 \quad (-7)
 \end{array}$$

$$\begin{array}{r}
 \textcircled{1}100 \quad (-4) \\
 + \textcircled{1}011 \quad (-5) \\
 \hline
 1\textcircled{0}111 \quad (+7)
 \end{array}$$

Detecting Signed Overflow

- Overflow occurs only in the two situations:
 - Adding two positive numbers and the sum is negative
 - Adding two negative numbers and the sum is positive
 - Can happen because of the fixed number of sum bits
- Overflow cannot occur if you add a positive number to a negative number. Do you see why?
- In two's complement addition/subtraction
 - If the two numbers have the same sign bit and the sum/difference has a different sign bit, then overflow
 - Or, if the carry out flags of the sign bit and the highest value bit are different

Overflow Detection

- For unsigned number
 - Add
 - The carry of 1 indicates overflow
 - Subtraction
 - The carry of 1 indicates that no correction of the result is required
 - The carry of 0 indicates that a correction of the result is required
- For signed number
 - $V = C_n \oplus C_{n-1}$


Important Flags

- Zero flag (ZF)
 - $ZF = 1$ means the result is 0
 - Valid for both unsigned and signed operations
- Sign flag (SF/NF)
 - The sign of the result, i.e., S_{n-1}
 - Valid for signed operations
- Carry/borrow flag (CF)
 - If $CF = 1$
 - Carry for addition, i.e., C_{out}
 - Borrow for subtraction, i.e., $\sim C_{out}$
 - Valid for unsigned operations
- Overflow flag (OF)
 - Valid for signed operations

Adders with Flags

- ZF, SF, CF and OF

Symbol

 


Overview

- Addition
- Subtraction
- Arithmetic logic unit (ALU)
- Multiplication
- Division
- Floating number operations


What is ALU?

 - An arithmetic-logic unit, or ALU, performs many different arithmetic and logic operations. The ALU is the “heart” of a processor—you could say that everything else in the CPU is there to support the ALU.
- Two methods constitute the ALU
 - extended the adder
 - Parallel redundant select




A Simple Example: 1-Bit ALU with 3 OPs

$F_{1:0}$	Function
00	$A \& B$
01	$A B$
10	$A + B$
11	not used

 


```
module ALU(  
    input [3:0] a, b,  
    input [1:0] aluop,  
    input cin,  
    output [3:0] f,  
    output OF, SF, ZF, CF,  
    output cout  
);  
    wire [3:0] sum;  
    CLA_FLAGS(a, b, cin, sum, OF, SF, ZF,  
    CF, cout);  
    always @(*) begin  
        case(aluop)  
            2'b00: f = a & b;  
            2'b01: f = a | b;  
            2'b10: f = sum;  
            default: f = 0;  
        endcase  
    end  
endmodule
```

N-Bit ALU with 8 OPs

 


ALU Control Lines	Function
000	And
001	Or
010	Add
110	Sub
111	SLT
100	nor
101	srl
011	xor

 

Set Less Than (SLT) Example

- Configure 32-bit ALU for SLT operation: $A = 25$ and $B = 32$

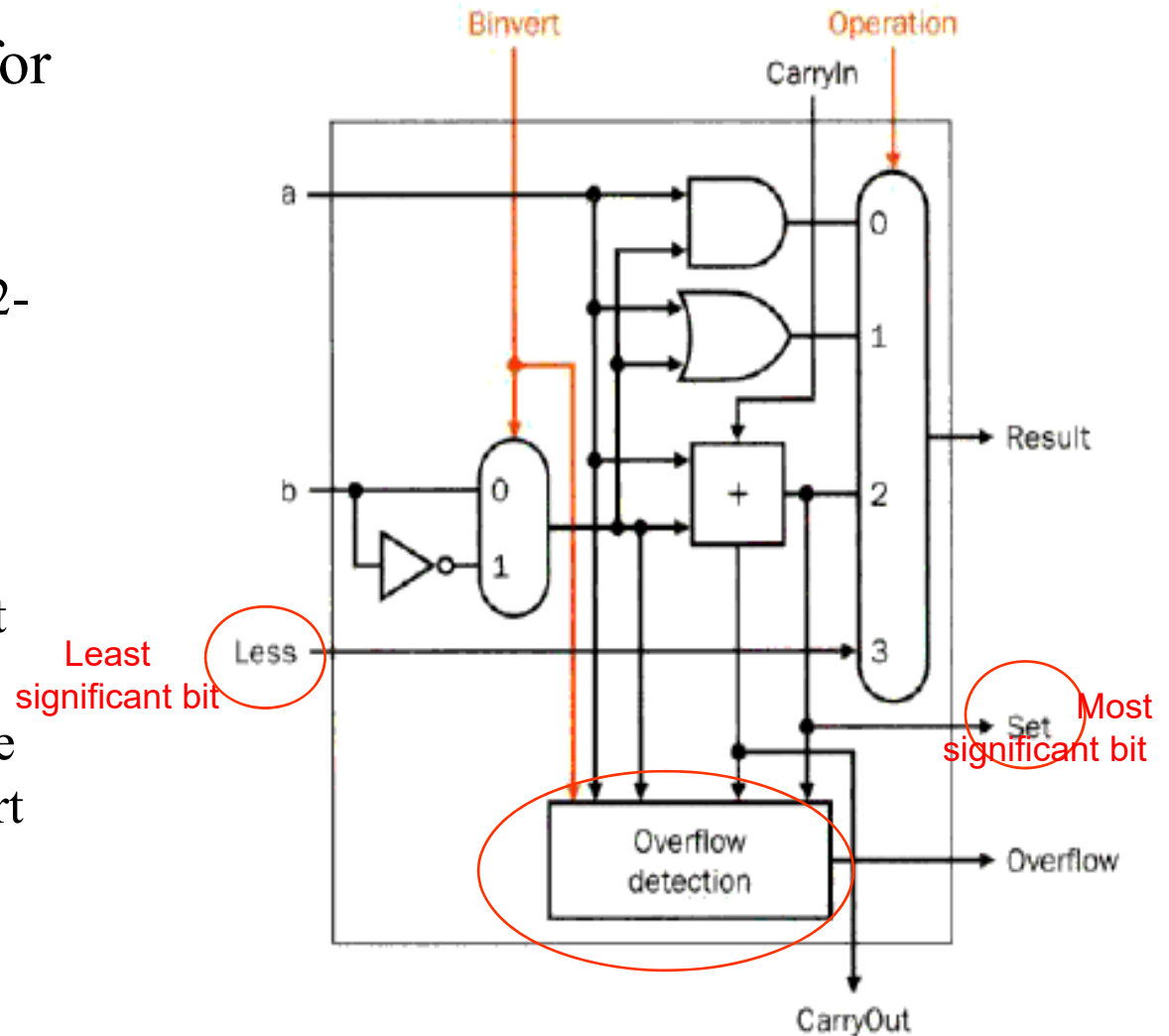
- $A < B$, so Y should be 32-bit representation of 1 (0x00000001)
- `slt rd,rs,rt`
- If $rs < rt$, $rd=1$, else $rd=0$
- For rd , all bits = 0 except the least significant
- Subtraction ($rs - rt$), if the result is negative $\rightarrow rs < rt$
- **Use of sign bit as indicator**



Set Less Than (SLT)

- Configure 32-bit ALU for SLT operation: $A = 25$ and $B = 32$

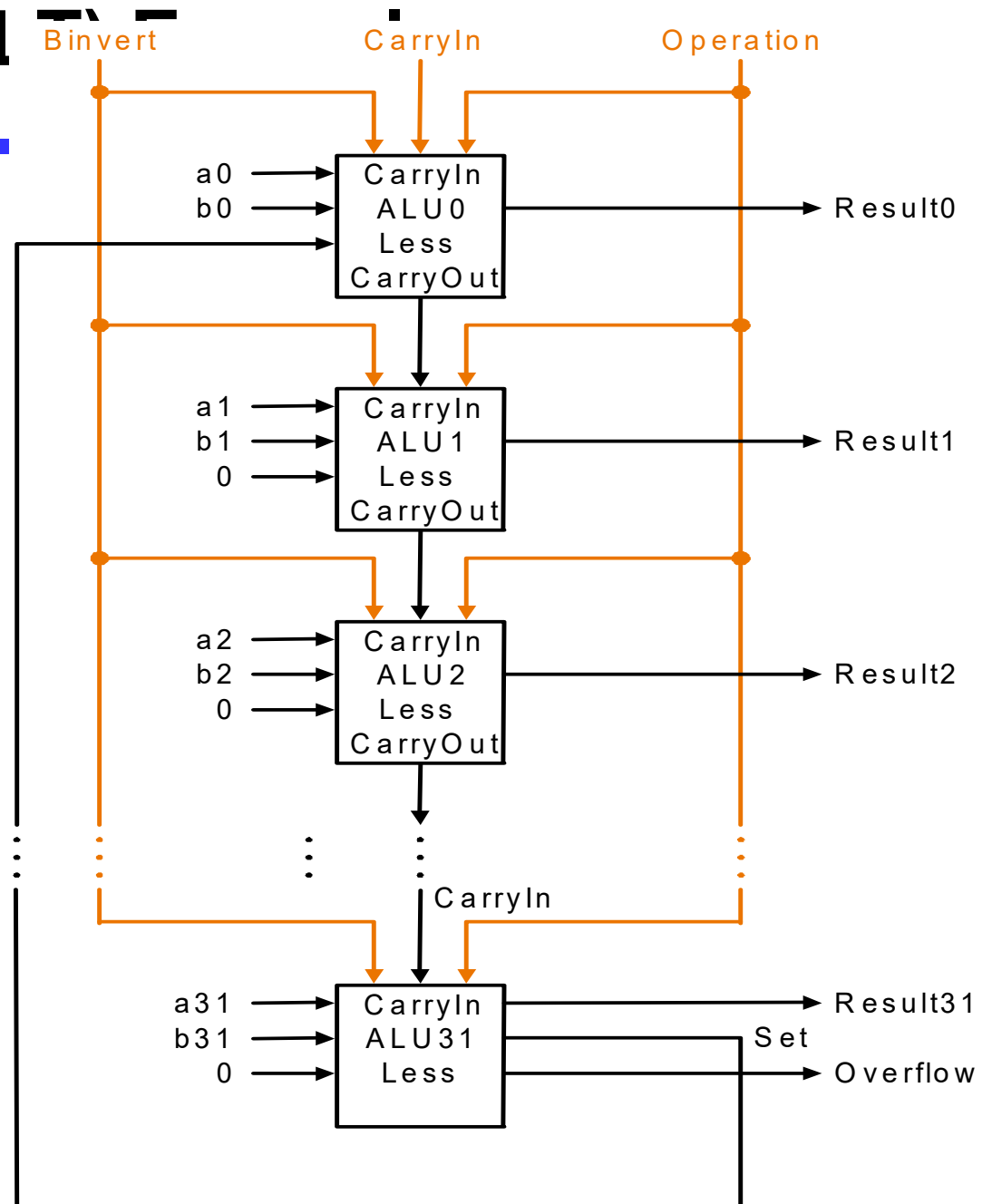- $A < B$, so Y should be 32-bit representation of 1 ($0x00000001$)
- $F_{2:0} = 111$
 - $F_2 = 1$ (adder acts as subtracter), so $25 - 32 = -7$
 - -7 has 1 in the most significant bit ($S_{31} = 1$)
 - $F_{1:0} = 11$ multiplexer selects $Y = S_{31}$ (zero extended) = $0x00000001$.



Various Use of Shifters

- Logical shifter: shifts value to left or right and fills empty spaces with 0's
 - $11001 \gg 2 = 00110$
 - $11001 \ll 2 = 00100$
- Arithmetic shifter: same as logical shifter, but on right shift, fills empty spaces with the old most significant bit (MSB).
 - $11001 \ggg 2 = 11110$
 - $11001 \lll 2 = 00100$
- Rotator: rotates bits in a circle, such that bits shifted off one end are shifted into the other end
 - $11001 \text{ ROR } 2 = 01110$
 - $11001 \text{ ROL } 2 = 00111$

Shifters as Multipliers and Dividers


- $A \ll N = A \times 2^N$
 - E.g., $00001 \ll 2 = 00100$ ($1 \times 2^2 = 4$)
 - E.g., $11101 \ll 2 = 10100$ ($-3 \times 2^2 = -12$)

- $A \ggg N = A \div 2^N$
 - E.g., $01000 \ggg 2 = 00010$ ($8 \div 2^2 = 2$)
 - E.g., $10000 \ggg 2 = 11100$ ($-16 \div 2^2 = -4$)

Recall the Design of A Shifter

- Bidirectional shift registers with parallel load
 - Data from Bus B can be transferred to the register in parallel and then shifted to the right, the left, or not at all.
 - A clock pulse loads the output of Bus B into the shift register, and a second clock pulse performs the shift.
 - Finally, a third clock pulse transfers the data from the shift register to the selected destination register.
- Alternatively, the transfer from a source register to a destination register can be done using *only one clock pulse* if the shifter is implemented *as a combinational circuit*
 - Because of the faster operation that results from the use of one clock pulse instead of three, this is the preferred method.
 - In a combinational shifter, the signals propagate through the gates without the need for a clock pulse.
 - Hence, the only clock needed for a shift in the datapath is for loading the data from Bus H into the selected destination register.

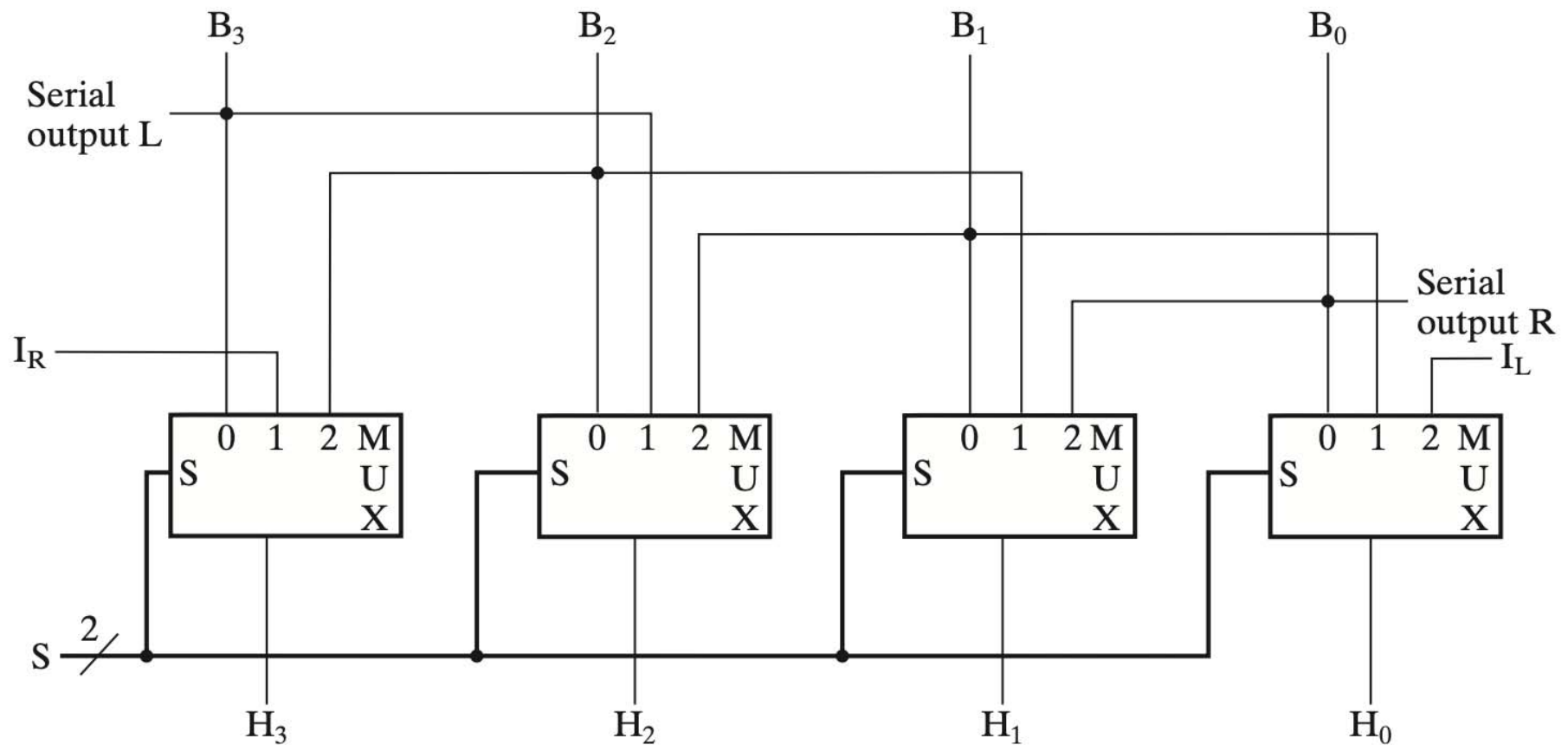
Shifter Design as A Combinational Circuit



4-Bit Barrel Shifter (ROL)

Function Table for 4-Bit Barrel Shifter

Select		Output				Operation
S_1	S_0	Y_3	Y_2	Y_1	Y_0	
0	0	D_3	D_2	D_1	D_0	No rotation
0	1	D_2	D_1	D_0	D_3	Rotate one position
1	0	D_1	D_0	D_3	D_2	Rotate two positions
1	1	D_0	D_3	D_2	D_1	Rotate three positions

 

Overview

- Addition
- Subtraction
- Arithmetic logic unit (ALU)
- **Multiplication**
- Division
- Floating number operations

Multiplication

- More complicated than addition
 - A straightforward implementation will involve shifts and adds
- More complex operation can lead to
 - More area (on silicon) and/or
 - More time (multiple cycles or longer clock cycle time)
- Let's begin from a simple, straightforward method

Decimal vs. Binary Multiplication

- Partial products formed by multiplying a single digit of the multiplier with multiplicand
- Shifted partial products summed to form result

Decimal

$$\begin{array}{r} 230 \\ \times 42 \\ \hline 460 \\ + 920 \\ \hline 9660 \end{array}$$

multiplicand
multiplier

partial
products

result

$$230 \times 42 = 9660$$

Binary

$$\begin{array}{r} 0101 \\ \times 0111 \\ \hline 0101 \\ 0101 \\ 0101 \\ + 0000 \\ \hline 0100011 \end{array}$$

$$5 \times 7 = 35$$

Unsigned Multiplication: 4-bit X 4-bit

Multiplication

	a_3	a_2	a_1	a_0	\leftarrow <i>Multiplicand</i>
\times	b_3	b_2	b_1	b_0	\leftarrow <i>Multiplier</i>
<hr/>					
		a_3b_0	a_2b_0	a_1b_0	a_0b_0
		a_3b_1	a_2b_1	a_1b_1	a_0b_1
	a_3b_2	a_2b_2	a_1b_2	a_0b_2	
a_3b_3	a_2b_3	a_1b_3	a_0b_3		
<hr/>					
	\dots	$a_1b_0 + a_0b_1$	a_0b_0	\leftarrow <i>Product</i>	

} *Partial products*

Unsigned Multiplication: M-bit X N-bit

$$A = a_{m-1} \dots a_1 a_0 \quad B = b_{n-1} \dots b_1 b_0$$

$$a = \sum_{i=0}^{m-1} a_i 2^i \quad b = \sum_{j=0}^{n-1} b_j 2^j$$



$$p = ab = \left(\sum_{i=0}^{m-1} a_i 2^i \right) \left(\sum_{j=0}^{n-1} b_j 2^j \right) = \sum_{i=0}^{m-1} \sum_{j=0}^{n-1} (a_i b_j) 2^{i+j} = \sum_{k=0}^{m+n-1} p_k 2^k$$

$$\begin{array}{r}
 \begin{array}{cccccc}
 & & a_{m-1} & a_{m-2} & \dots & a_1 & a_0 & = A \\
 \times &) & & b_{n-1} & \dots & b_1 & b_0 & = B \\
 \hline
 & & a_{m-1}b_0 & a_{m-2}b_0 & \dots & a_1b_0 & a_0b_0 & \\
 & & a_{m-1}b_1 & a_{m-2}b_1 & \dots & a_1b_1 & a_0b_1 & \\
 & & \cdot & \cdot & \cdot & \cdot & \cdot & \\
 & & \cdot & \cdot & \cdot & \cdot & \cdot & \\
 + &) & a_{m-1}b_{n-1} & a_{m-2}b_{n-1} & \dots & a_1b_{n-1} & a_0b_{n-1} & \\
 \hline
 p_{m+n-1} & p_{m+n-2} & p_{m+n-3} & \dots & p_{n-1} & \dots & p_1 & p_0 = P
 \end{array}
 \end{array}$$

Straightforward Algorithm

```
      01010010 (multiplicand)
x 01101101 (multiplier)
-----
      01010010
      00000000
     01010010
    01010010
   00000000
  01010010
 01010010
00000000
-----
010001011101010
```

Implementation 1

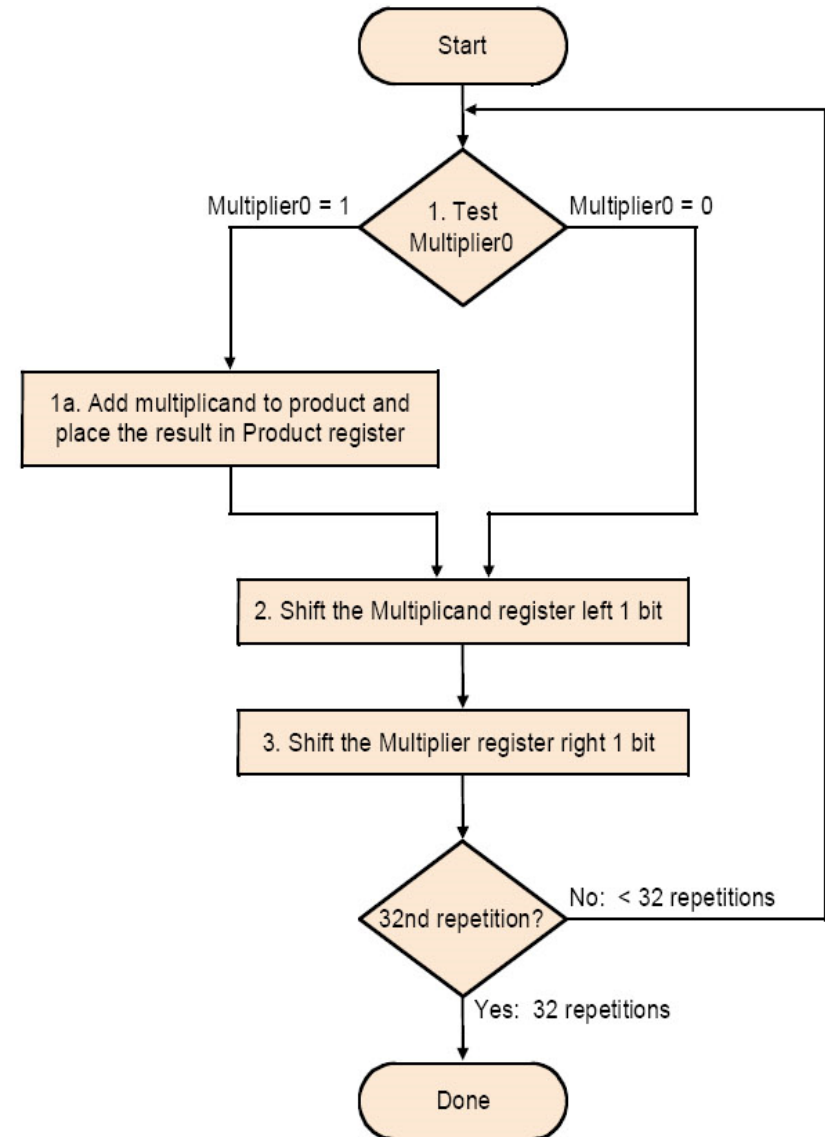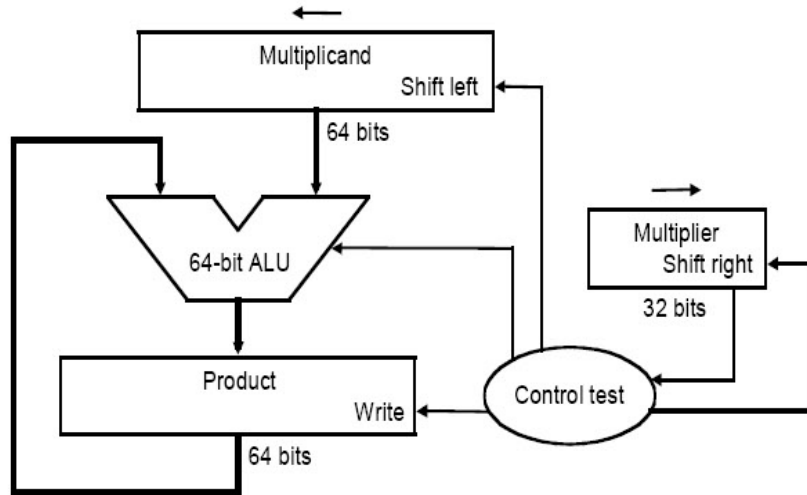

Example of Implementation 1


- Let's do 0010 x 0110 (2 x 6), unsigned

Iteration	Implementation 1			
	Step	Multiplier	Multiplicand	Product
0	initial values	0110	0000 0010	0000 0000
1	1: 0 -> no op	0110	0000 0010	0000 0000
	2: Multiplier shift right/ Multiplicand shift left	011	0000 0100	0000 0000
2	1: 1 -> product = product + multiplicand	011	0000 0100	0000 0100
	2: Multiplier shift right/ Multiplicand shift left	01	0000 1000	0000 0100
3	1: 1 -> product = product + multiplicand	01	0000 1000	0000 1100
	2: Multiplier shift right/ Multiplicand shift left	0	0001 0000	0000 1100
4	1: 0 -> no op	0	0001 0000	0000 1100
	2: Multiplier shift right/Multiplicand shift left		0010 0000	


Drawbacks

- The ALU is twice as wide as necessary
- The multiplicand register takes twice as many bits as needed
- The product register won't need $2n$ bits till the last step
 - Being filled
- The multiplier register is being emptied during the process

Implementation 2

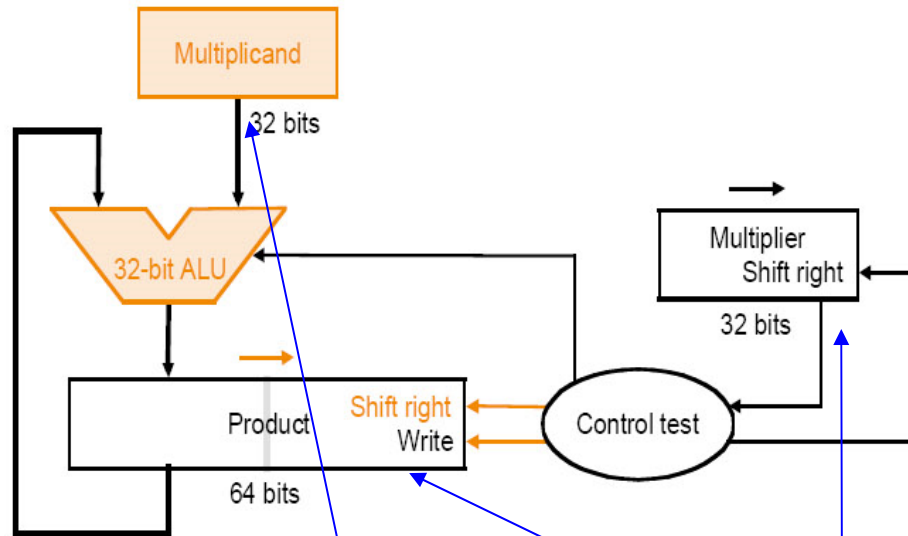

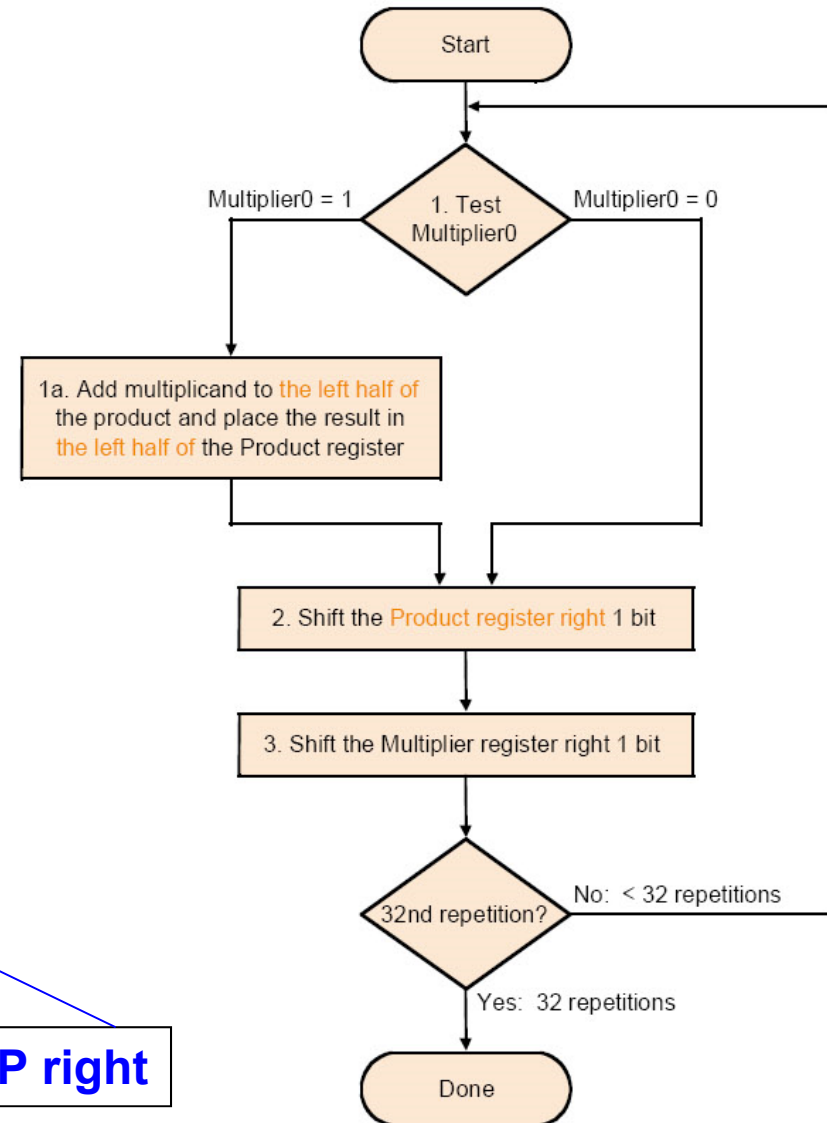Multiplicand stationary - Multiplier right - PP right




Example of Implementation 2

- Let's do 0010 x 0110 (2 x 6), unsigned

Iteration	Implementation 2			
	Step	Multiplier	Multiplicand	Product
0	initial values	0110	0010	0000 _{xxxx}
1	1: 0 -> no op	0110	0010	0000 _{xxxx}
	2: Multiplier shift right/ Product shift right	_x 011	0010	0000 0 _{xxx}
2	1: 1 -> product = product + multiplicand	_x 011	0010	0010 0 _{xxx}
	2: Multiplier shift right/ Product shift right	_{xx} 01	0010	0001 00 _{xx}
3	1: 1 -> product = product + multiplicand	_{xx} 01	0010	0011 00 _{xx}
	2: Multiplier shift right/ Product shift right	_{xxx} 0	0010	0001 100 _x
4	1: 0 -> no op	_{xxx} 0	0010	0001 100 _x
	2: Multiplier shift right/ Product shift right	_{xxxx}	0010	0000 1100

Implementation 3

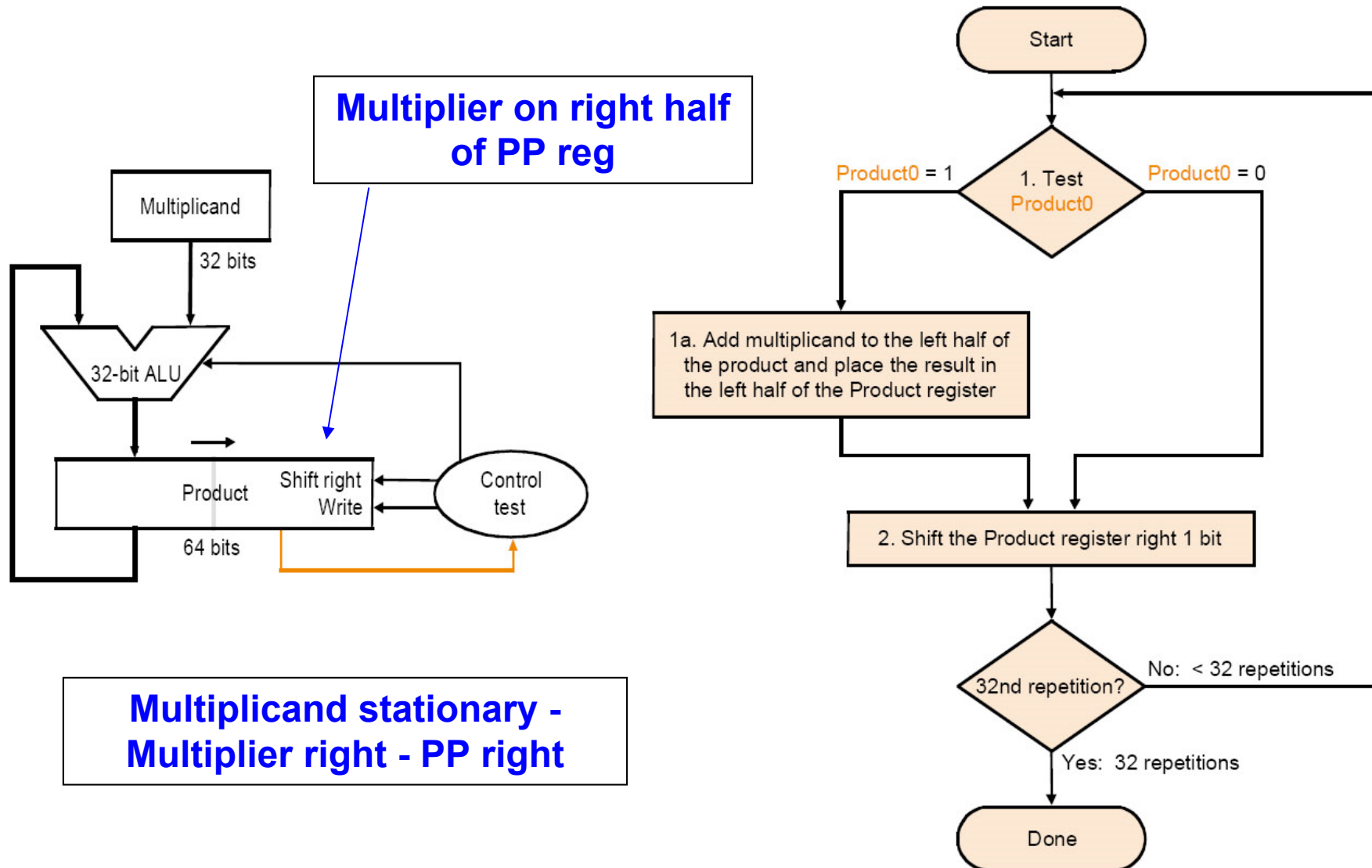

Example of Implementation 3

- Let's do 0010 x 0110 (2 x 6), unsigned

Iteration	Implementation 3			
	Step	Multiplier	Multiplicand	Product Multiplier
0	initial values	0110	0010	0000 0110
1	1: 0 -> no op	0110	0010	0000 0110
	2: Multiplier shift right/ Product shift right	_x 011	0010	0000 0011
2	1: 1 -> product = product + multiplicand	_x 011	0010	0010 0011
	2: Multiplier shift right/ Product shift right	_{xx} 01	0010	0001 0001
3	1: 1 -> product = product + multiplicand	_{xx} 01	0010	0011 0001
	2: Multiplier shift right/ Product shift right	_{xxx} 00	0010	0001 1000
4	1: 0 -> no op	_{xxxx} 0	0010	0001 1000
	2: Multiplier shift right/ Product shift right	_{xxxx}	0010	0000 1100

Signed Multiplication

- Basic approach:
 - Store the signs of the operands
 - Convert signed numbers to unsigned numbers (most significant bit (MSB) = 0)
 - Perform multiplication
 - If sign bits of operands are equal
 sign bit = 0, else
 sign bit = 1
- Improved method:
 Booth's Algorithm

Assumption: addition and subtraction are available

Principle -- Decomposable multiplication

- Assumes: $Z = y \times 10111100$

$$Z = y(10000000 + 111100 + 100 - 100)$$

$$= y(1 \times 2^7 + 1000000 - 100)$$

$$= y(1 \times 2^7 + 1 \times 2^6 - 2^2)$$


$$= y(1 \times 2^7 + 1 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 + 0 \times 2^1 + 0 \times 2^0 - 1 \times 2^2)$$

$$= y(1 \times 2^7 + 1 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 - 1 \times 2^2 + 0 \times 2^1 + 0 \times 2^0)$$

$$= y \times 2^7 + y \times 1 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 0 \times 2^3 + 0 \times 2^2 - y \times 2^2 + 0 \times 2^1 + 0 \times 2^0$$

Booth's Algorithm

 - Idea: If you have a sequence of '1's
 - subtract at first '1' in multiplier
 - shift for the sequence of '1's
 - add where prior step had last '1'



- Result:
 - Possibly less additions and more shifts
 - Faster, if shifts are faster than additions

Booth's Algorithm

Current bit	Bit to right	Explanation	Example	Operation
1	0	Begins run of '1'	0000111 1 000	Subtract
1	1	Middle of run of '1'	000011 11 000	Nothing
0	1	End of a run of '1'	000 01 111000	Add
0	0	Middle of a run of '0'	0 00 01111000	Nothing

Example 1 of Booth's Algorithm

- Let's do 0010×1101 (2×-3)

Iteration	Implementation 3		
	Step	Multiplicand	Product
0	initial values	0010	0000 110 1 0
1	10 -> product = product – multiplicand	0010	1110 1101 0
	shift right		1111 011 0 1
2	01 -> product = product + multiplicand	0010	0001 0110 1
	shift right		0000 101 1 0
3	10 -> product = product – multiplicand	0010	1110 1011 0
	shift right		1111 010 1 1
4	11 -> no op	0010	1111 0101 1
	shift right		1111 1010 1

Example 2 of Booth's Algorithm

- Negative multiplicand:
 - $-6 \times 6 = -36$
 - 1010×0110 , 0110 in Booth's encoding is $+0-0$
 - Hence:

1111 1010	$\times 0$	0000 0000
1111 0100	$\times -1$	0000 1100
1110 1000	$\times 0$	0000 0000
1101 0000	$\times +1$	1101 0000
	Final Sum:	1101 1100 (-36)

Example 3 of Booth's Algorithm

- Negative multiplier:
 - $-6 \times -2 = 12$
 - 1010×1110 , 1110 in Booth's encoding is $00-0$
 - Hence:

1111 1010	$\times 0$	0000 0000
1111 0100	$\times -1$	0000 1100
1110 1000	$\times 0$	0000 0000
1101 0000	$\times 0$	0000 0000
	Final Sum:	0000 1100 (12)

Summary

$$\begin{array}{r} 0\ 0\ 1\ 0\ 1\ 1 \\ 0\ 1\ 0\ 0\ 1\ 1 \\ \hline 0\ 0\ 1\ 0\ 1\ 1 \\ 0\ 0\ 1\ 0\ 1\ 1 \\ 0\ 0\ 0\ 0\ 0\ 0 \\ 0\ 0\ 0\ 0\ 0\ 0 \\ 0\ 0\ 1\ 0\ 1\ 1 \\ \hline 0\ 0\ 1\ 1\ 0\ 1\ 0\ 0\ 0\ 1 \end{array}$$

Benefit: Reducing the number of partial products

Take away: Booth encoding

Exercise


Unsigned Multiplication: $x=5, y=3$

Signed Multiplication: $x=5, y=-7$

Yet Another Option: Array Multiplier


				1	0	0	0
			x	1	0	0	1
				1	0	0	0
		0	0	0	0	0	
	0	0	0	0	0		
1	0	0	0				
1	0	0	1	0	0	0	0

 Adding all partial products simultaneously using an array of basic cells




4 x 4 Array Multiplier
 
$$\begin{array}{r}
 \begin{array}{cccc}
 & A_3 & A_2 & A_1 & A_0 \\
 \times & B_3 & B_2 & B_1 & B_0 \\
 \hline
 & A_3B_0 & A_2B_0 & A_1B_0 & A_0B_0 \\
 & A_3B_1 & A_2B_1 & A_1B_1 & A_0B_1 \\
 & A_3B_2 & A_2B_2 & A_1B_2 & A_0B_2 \\
 + & A_3B_3 & A_2B_3 & A_1B_3 & A_0B_3 \\
 \hline
 P_7 & P_6 & P_5 & P_4 & P_3 & P_2 & P_1 & P_0
 \end{array}
 \end{array}$$



16-bit Array Multiplier

 

Conceptually straightforward

Fairly expensive hardware, integer multiplies relatively rare

Most used in array address calc: replace with shifts

Overview

- Addition
- Subtraction
- Arithmetic logic unit (ALU)
- Multiplication
- **Division**
- Floating number operations

Unsigned Division


- Again, back to 3rd grade ($74 \div 8 = 9 \text{ rem } 2$)

$$\begin{array}{r}
 \begin{array}{cccc}
 & & & 1 & 0 & 0 & 1 & \text{Quotient} \\
 \text{Divisor} & 1 & 0 & 0 & 0 & \overline{) 1 & 0 & 0 & 1 & 0 & 1 & 0} & \text{Dividend} \\
 & & & - & 1 & 0 & 0 & 0 & & & & \\
 & & & \hline
 & & & & 1 & 0 & & & & & & \\
 & & & & & 1 & 0 & 1 & & & & \\
 & & & & & 1 & 0 & 1 & 0 & & & \\
 & & & & & - & 1 & 0 & 0 & 0 & & \\
 & & & & & \hline
 & & & & & & & 1 & 0 & & \text{Remainder}
 \end{array}
 \end{array}$$


Unsigned Division

- How does hardware know if division fits?
 - Condition: if remainder \geq divisor
 - Use subtraction: (remainder – divisor) ≥ 0
- OK, so if it fits, what do we do?
 - $\text{Remainder}_{n+1} = \text{Remainder}_n - \text{divisor}$
- What if it doesn't fit?
 - Have to restore original remainder
- Called **restoring division**

Implementation 1

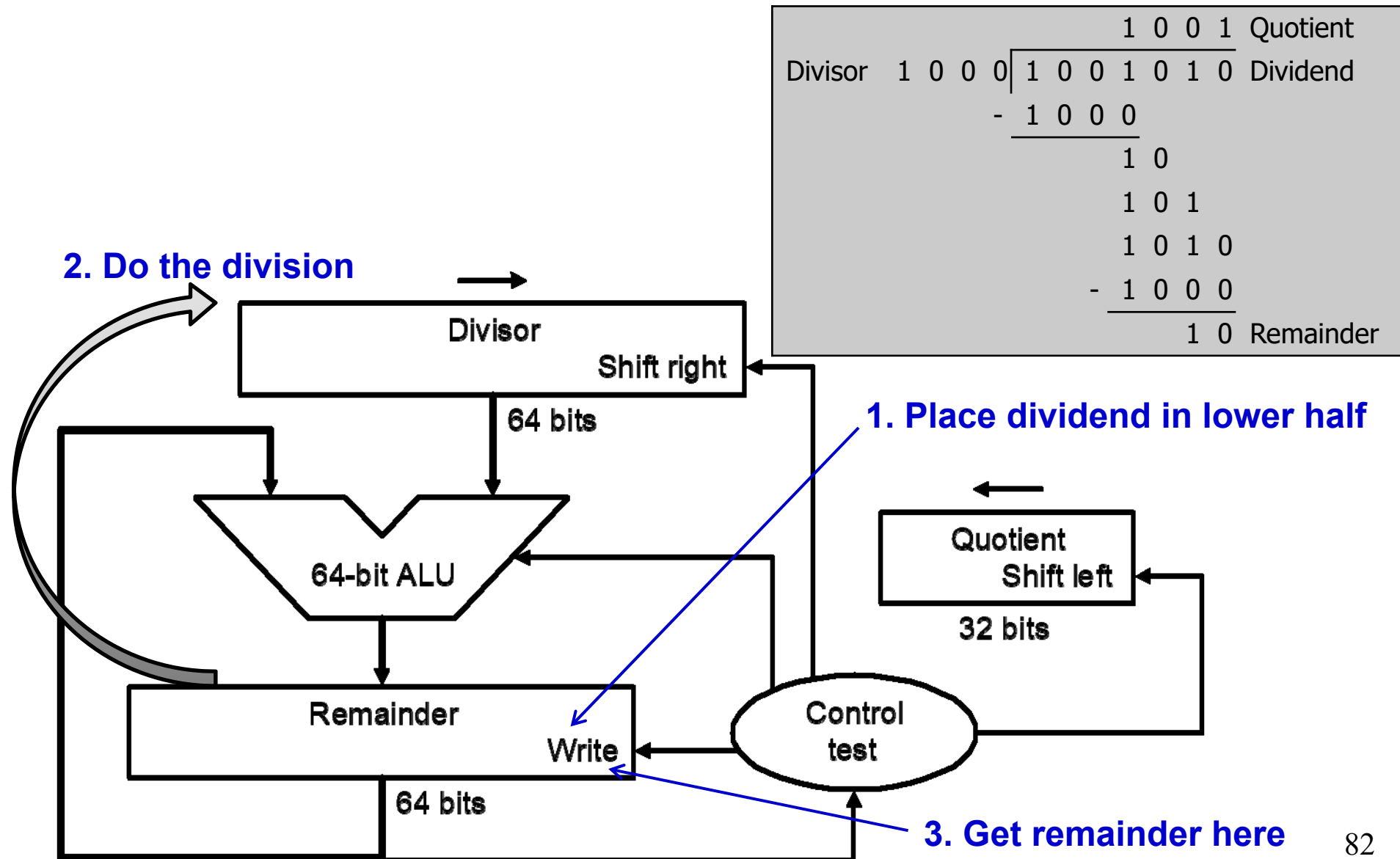

Implementation 1

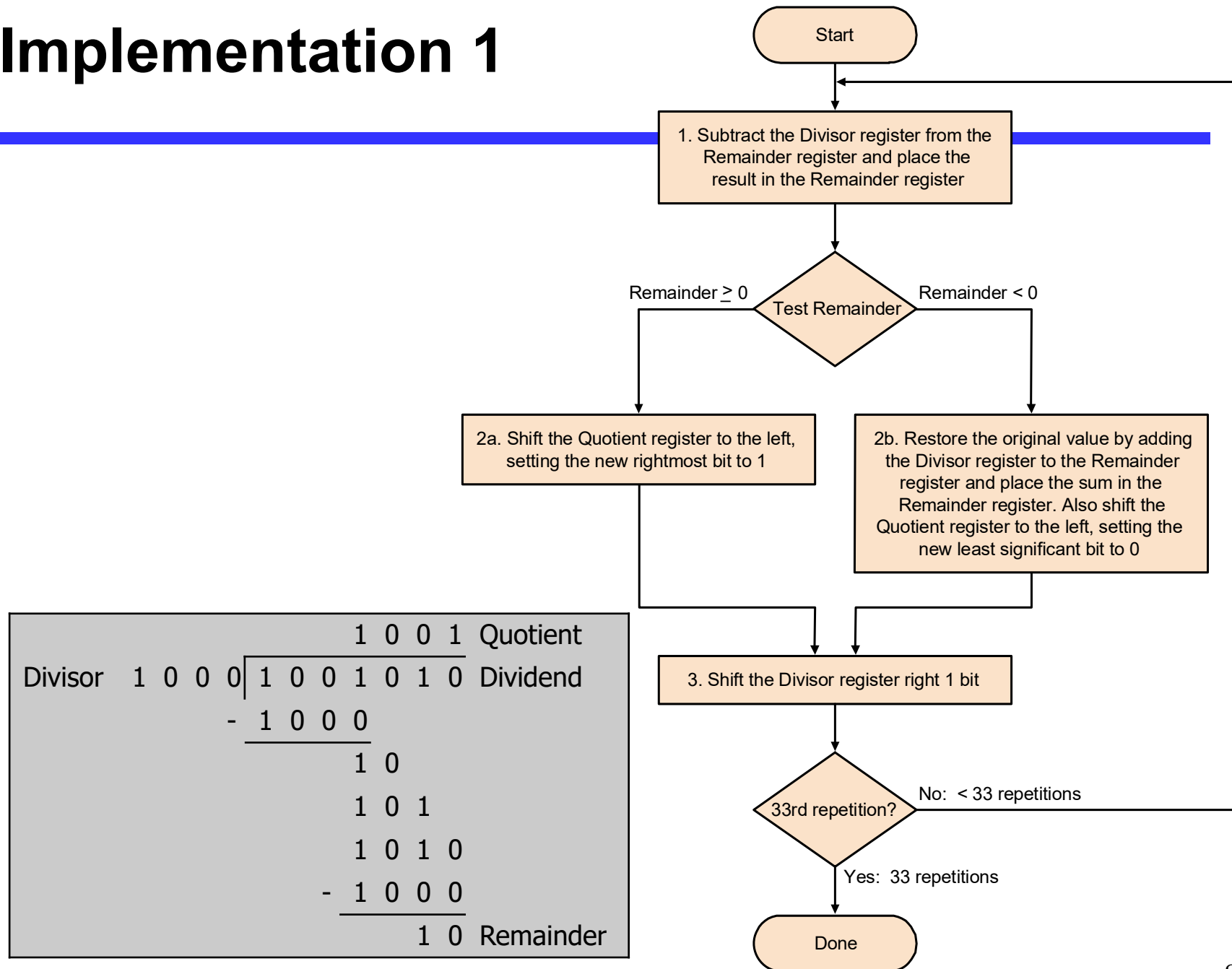

Example of Implementation 1


- Let's do $7 \div 2$

Iteration	Step	Quotient	Divisor	Remainder
0	Initial values	0000	0010 0000	0000 0111
1	1: Rem=Rem-Div	0000	0010 0000	1110 0111
	2b: Rem<0=>+Div, sll Q, Q ₀ =0	0000	0010 0000	0000 0111
	3: Shift Div right	0000	0001 0000	0000 0111
2	1: Rem=Rem-Div	0000	0001 0000	1111 0111
	2b: Rem<0=>+Div, sll Q, Q ₀ =0	0000	0001 0000	0000 0111
	3: Shift Div right	0000	0000 1000	0000 0111
3	1: Rem=Rem-Div	0000	0000 1000	1111 1111
	2b: Rem<0=>+Div, sll Q, Q ₀ =0	0000	0000 1000	0000 0111
	3: Shift Div right	0000	0000 0100	0000 0111
4	1: Rem=Rem-Div	0000	0000 0100	0000 0011
	2a: Rem≥0=> sll Q, Q ₀ =1	0001	0000 0100	0000 0011
	3: Shift Div right	0001	0000 0010	0000 0011
5	1: Rem=Rem-Div	0001	0000 0010	0000 0001
	2a: Rem≥0=> sll Q, Q ₀ =1	0011	0000 0010	0000 0001
	3: Shift Div right	0011	0000 0001	0000 0001


Division Improvements

- Skip first subtract
 - Can't shift '1' into quotient anyway
 - Hence shift first, then subtract
 - Undo extra shift at end
- Hardware similar to multiplier
 - Can store quotient in remainder register
 - Only need 32-bit ALU
 - Shift remainder left vs. divisor right

Implementation 2

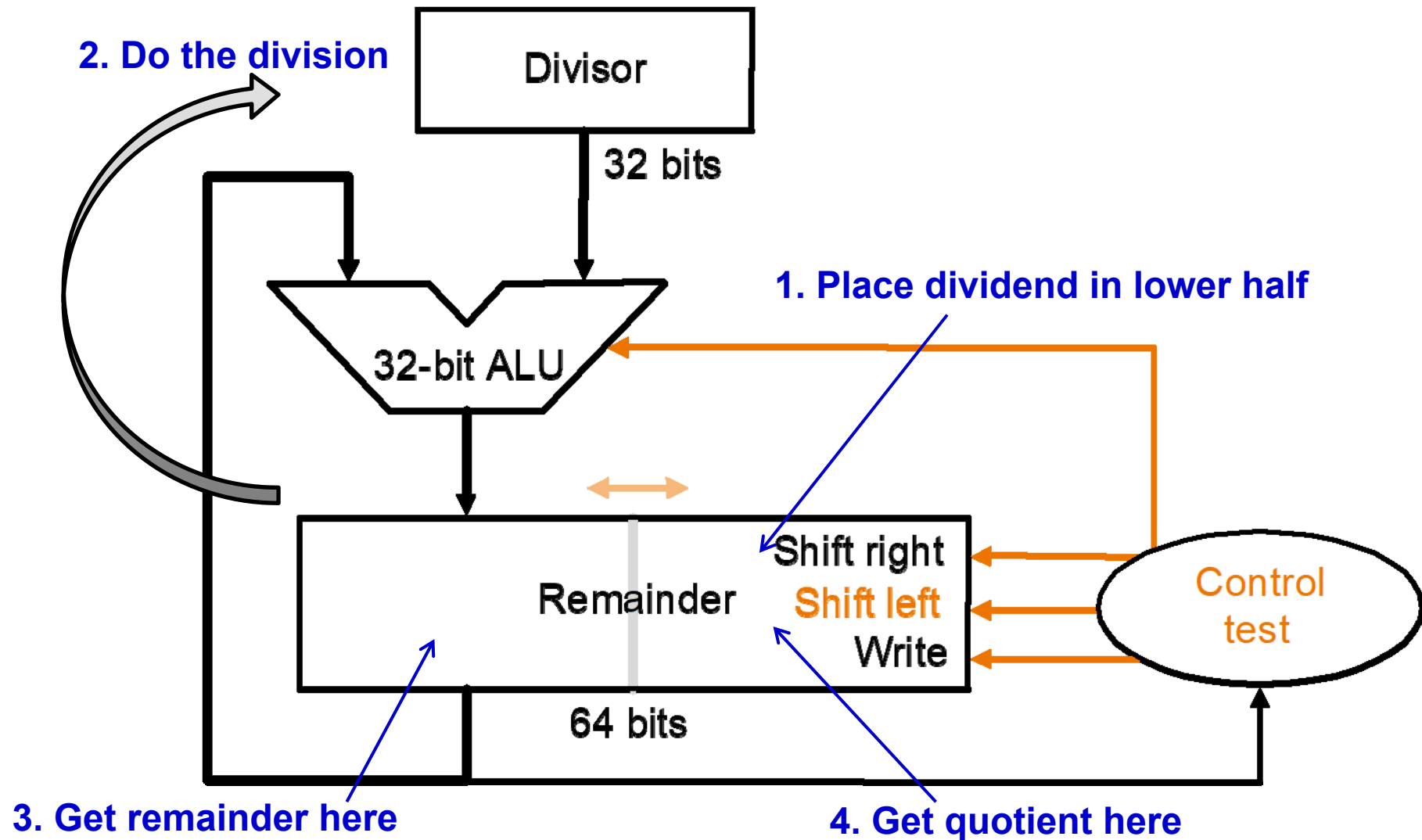

Implementation 2

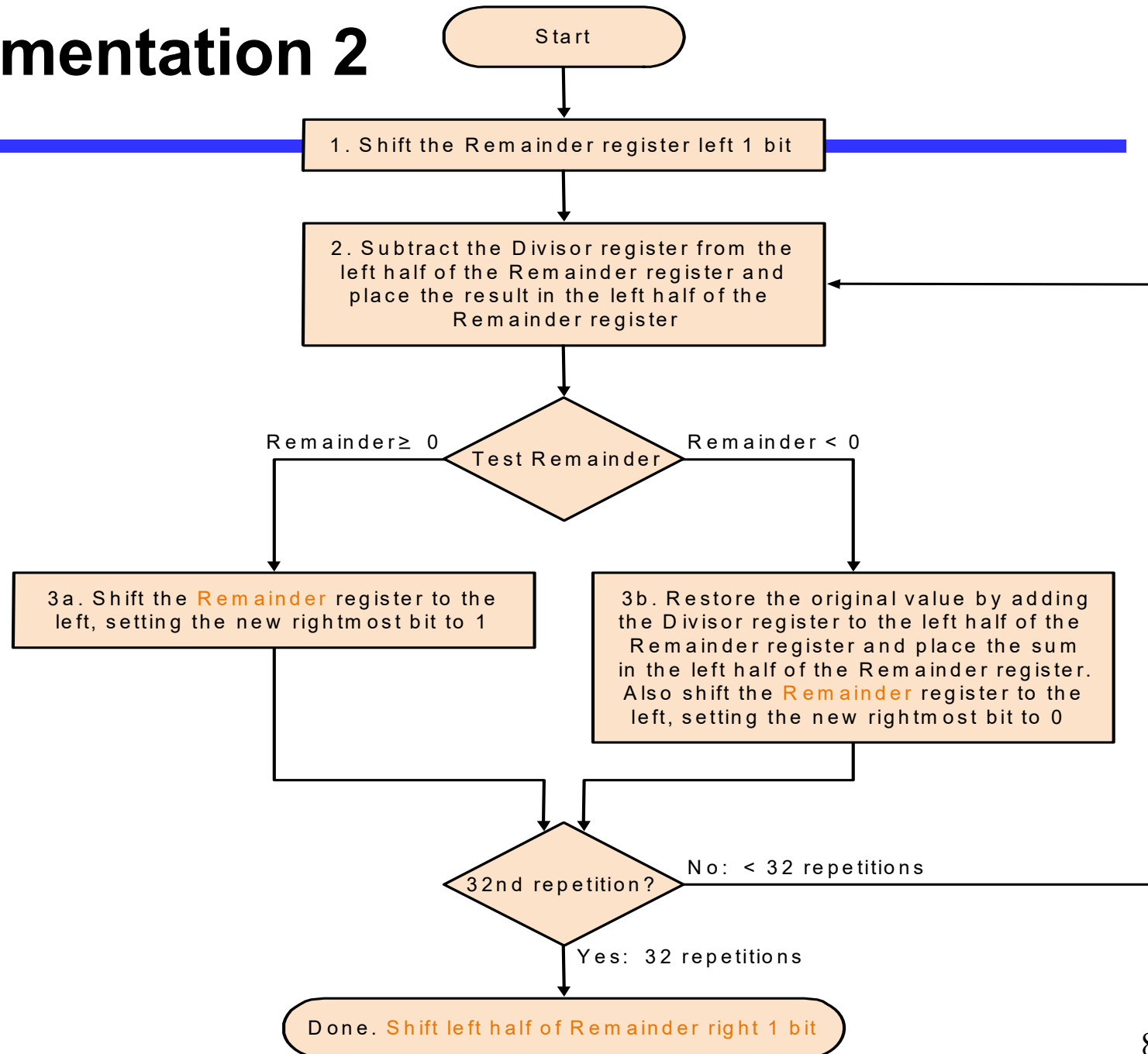

Restoring Division

Iteration	Divisor	Divide algorithm	
		Step	Remainder
0	0010	Initial values	0000 0111
	0010	Shift Rem left 1	0000 1110
1	0010	2: Rem = Rem - Div	1110 1110
	0010	3b: Rem < 0 \Rightarrow + Div, sll R, R0 = 0	0001 1100
2	0010	2: Rem = Rem - Div	1111 1100
	0010	3b: Rem < 0 \Rightarrow + Div, sll R, R0 = 0	0011 1000
3	0010	2: Rem = Rem - Div	0001 1000
	0010	3a: Rem \geq 0 \Rightarrow sll R, R0 = 1	0011 0001
4	0010	2: Rem = Rem - Div	0001 0001
	0010	3a: Rem \geq 0 \Rightarrow sll R, R0 = 1	0010 0011
Done	0010	shift left half of Rem right 1	0001 0011

Further Improvements

- Division still takes:
 - 2 ALU cycles per bit position
 - 1 to check for divisibility (subtract)
 - One to restore (if needed)
- Can reduce to 1 cycle per bit
 - Called **non-restoring division**
 - Avoids restore of remainder when test fails

Non-Restoring Division

- Consider remainder to be restored:

$$R_i = 2 \times R_{i-1} - d < 0$$

- Since R_i is negative, we must restore it, right?
- Well, maybe not. Consider next step $i+1$:

$$R_{i+1} = 2 \times (R_i) - d = 2 \times (R_i - d) + d$$

- Hence, we can compute R_{i+1} by not restoring R_i , and adding d instead of subtracting d
 - Same value for R_{i+1} results
- Throughput of 1 bit per cycle

Non-Restoring Division

Iteration	Step	Divisor	Remainder
0	Initial values	0010	0000 0111
	Shift rem left 1	0010	0000 1110
1	2: Rem = Rem - Div	0010	1110 1110
	3b: Rem < 0 (add next), sll 0	0010	1101 1100
2	2: Rem = Rem + Div	0010	1111 1100
	3b: Rem < 0 (add next), sll 0	0010	1111 1000
3	2: Rem = Rem + Div	0010	0001 1000
	3a: Rem > 0 (sub next), sll 1	0010	0011 0001
4	Rem = Rem - Div	0010	0001 0001
	Rem > 0 (sub next), sll 1	0010	0010 0011
	Shift Rem right by 1	0010	0001 0011

What About Signed Division?

- The simplest solution is to remember the signs of the divisor and dividend and then negate the quotient if the signs disagree.
- However, $(-7) \div 2 = ?$
 - $(+7) \div (-2) = ?$
 - $(-7) \div (-2) = ?$
- The correctly signed division algorithm *negates the quotient if the signs of the operands are opposite and makes the sign of the nonzero remainder match the dividend.*

Overview

- Addition
- Subtraction
- Arithmetic logic unit (ALU)
- Multiplication
- Division
- Floating number operations

Floating point addition

- Example in decimal: system precision 4 digits

What is $9.999 \cdot 10^1 + 1.610 \cdot 10^{-1}$?

- Aligning the two numbers

$$9.999 \cdot 10^1$$

$$0.01610 \cdot 10^1 \rightarrow 0.016 \cdot 10^1 \quad \text{Truncation}$$

- Addition

$$\begin{array}{r} 9.999 \cdot 10^1 \\ + 0.016 \cdot 10^1 \\ \hline 10.015 \cdot 10^1 \end{array}$$

- Normalization

$$1.0015 \cdot 10^2$$

- Rounding

$$1.002 \cdot 10^2$$

Floating point addition steps


- Alignment
- The proper digits have to be added
- Addition of significands
- Normalization of the result
- Rounding

Example $y=0.5+(-0.4375)$ in binary


- $0.5_{10} = 1.000_2 \times 2^{-1}$
- $-0.4375_2 = -1.110_2 \times 2^{-2}$
- Step1: The fraction with lesser exponent is shifted right until matches
 $-1.110_2 \times 2^{-2} \rightarrow -0.111_2 \times 2^{-1}$
- Step2: Add the significands
$$\begin{array}{r} 1.000_2 \times 2^{-1} \\ +) - 0.111_2 \times 2^{-1} \\ \hline 0.001_2 \times 2^{-1} \end{array}$$
- Step3: Normalize the sum and checking for overflow or underflow
 $0.001_2 \times 2^{-1} \rightarrow 0.010_2 \times 2^{-2} \rightarrow 0.100_2 \times 2^{-3} \rightarrow 1.000_2 \times 2^{-4}$
- Step4: Round the sum
 $1.000_2 \times 2^{-4} = 0.0625_{10}$

Algorithm

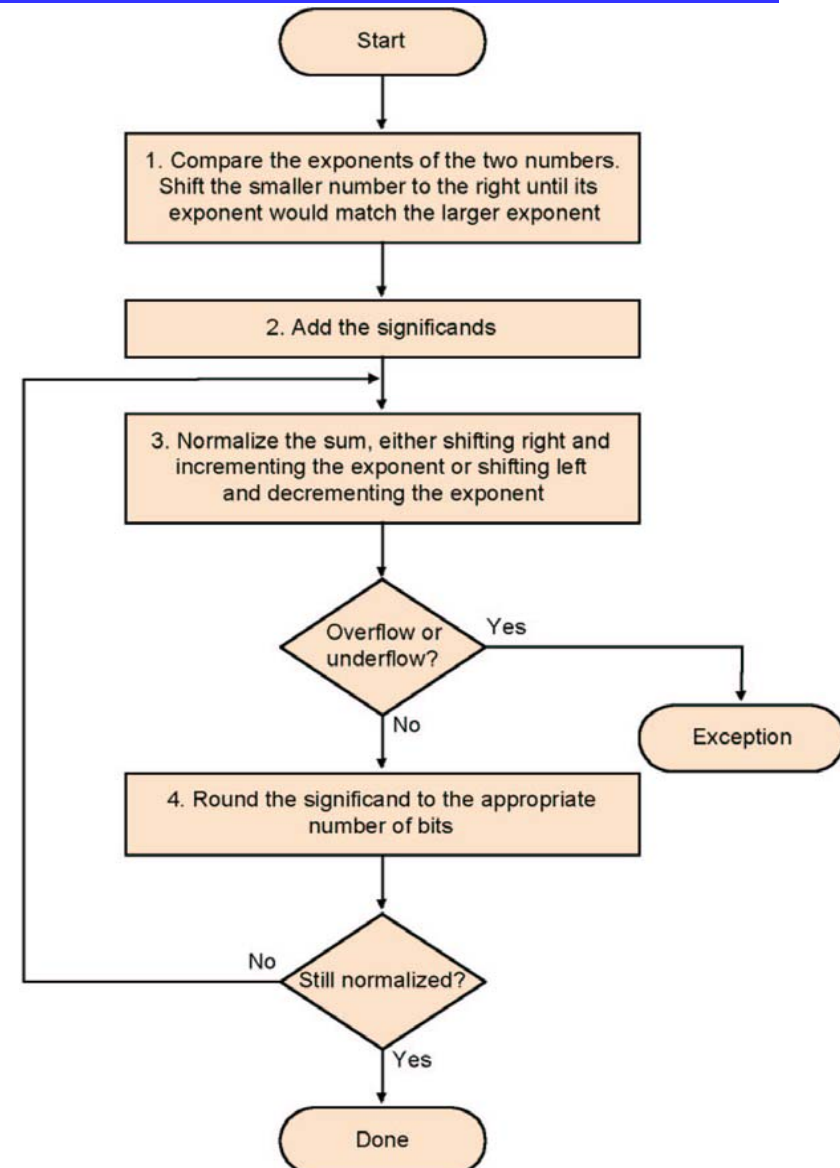- Normalize Significands
- Add Significands
- Normalize the sum
- Over/underflow
- Rounding
- Normalization



FP Adder Hardware

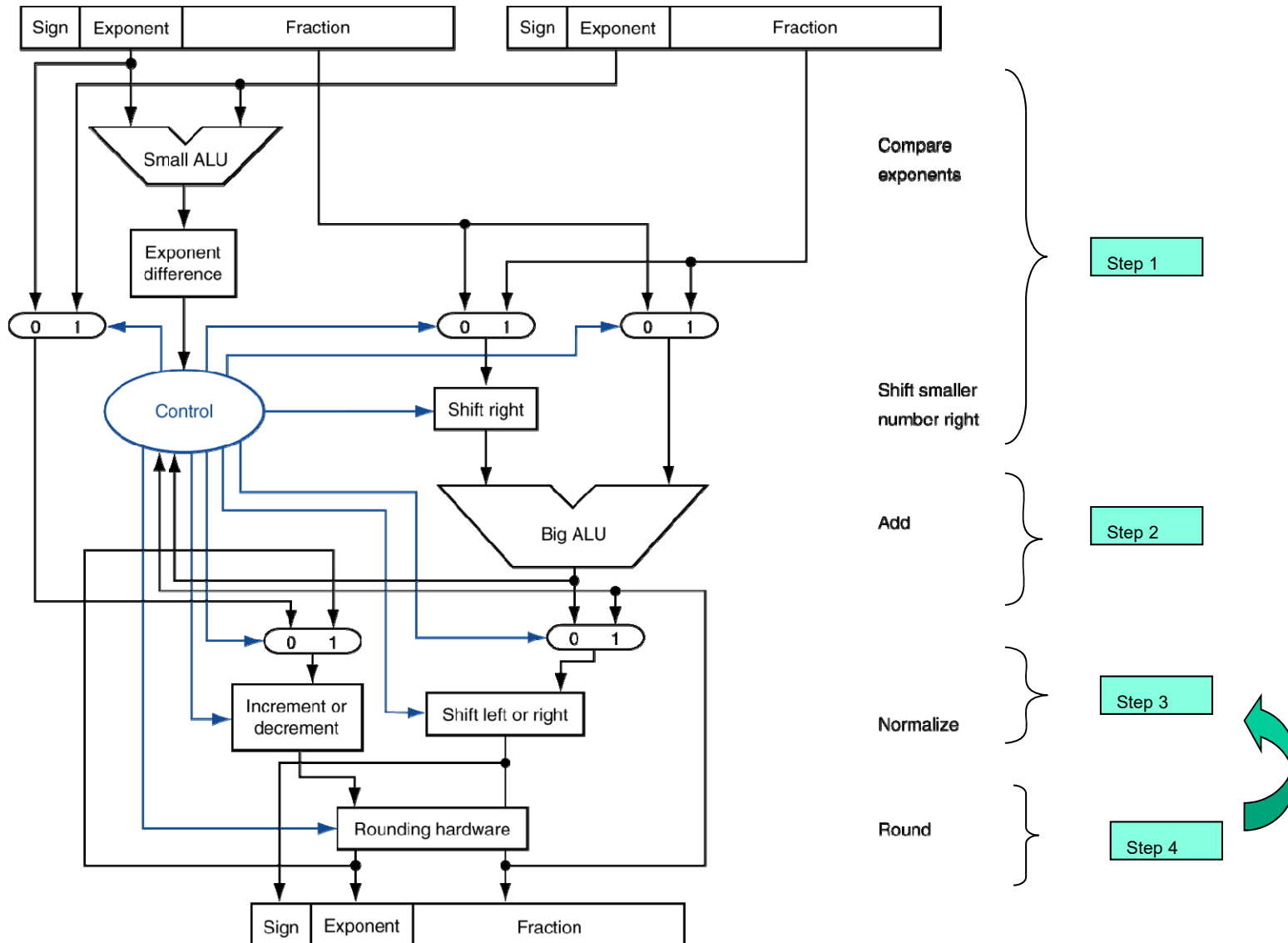

FP Adder Hardware

- Much more complex than integer adder
- Doing it in one clock cycle would take too long
 - Much longer than integer operations
 - Slower clock would penalize all instructions
- FP adder usually takes several cycles
 - Can be pipelined

Floating-Point Multiplication

- Consider a 4-digit decimal example
 - $1.110 \times 10^{10} \times 9.200 \times 10^{-5}$
- 1. Add exponents
 - For biased exponents, subtract bias from sum
 - New exponent = $10 + -5 = 5$
- 2. Multiply significands
 - $1.110 \times 9.200 = 10.212 \Rightarrow 10.212 \times 10^5$
- 3. Normalize result & check for over/underflow
 - 1.0212×10^6
- 4. Round and renormalize if necessary
 - 1.021×10^6
- 5. Determine sign of result from signs of operands
 - $+1.021 \times 10^6$

Floating Point Multiplication

- Composition of number from different parts

→ separate handling

$$(s1 \cdot 2^{e1}) \cdot (s2 \cdot 2^{e2}) = (s1 \cdot s2) \cdot 2^{e1+e2}$$

- Example

$$1 \ 10000010 \quad 000 \ 0000 \ 0000 \ 0000 \ 0000 \ 0000 = -1 \times 2^3$$

$$0 \ 10000011 \quad 000 \ 0000 \ 0000 \ 0000 \ 0000 \ 0000 = 1 \times 2^4$$

- Both significands are 1 → product = 1 → Sign=1

- Add the exponents, bias = 127


$$\begin{array}{r} 10000010 \\ +10000011 \\ \hline 110000101 \end{array}$$

Correction: $110000101 - 01111111 = 10000110 = 134 = 127 + 3 + 4$

- The result: $1 \ 10000110 \ 000 \ 0000 \ 0000 \ 0000 \ 0000 \ 0000 = -1 \times 2^7$

Multiplication

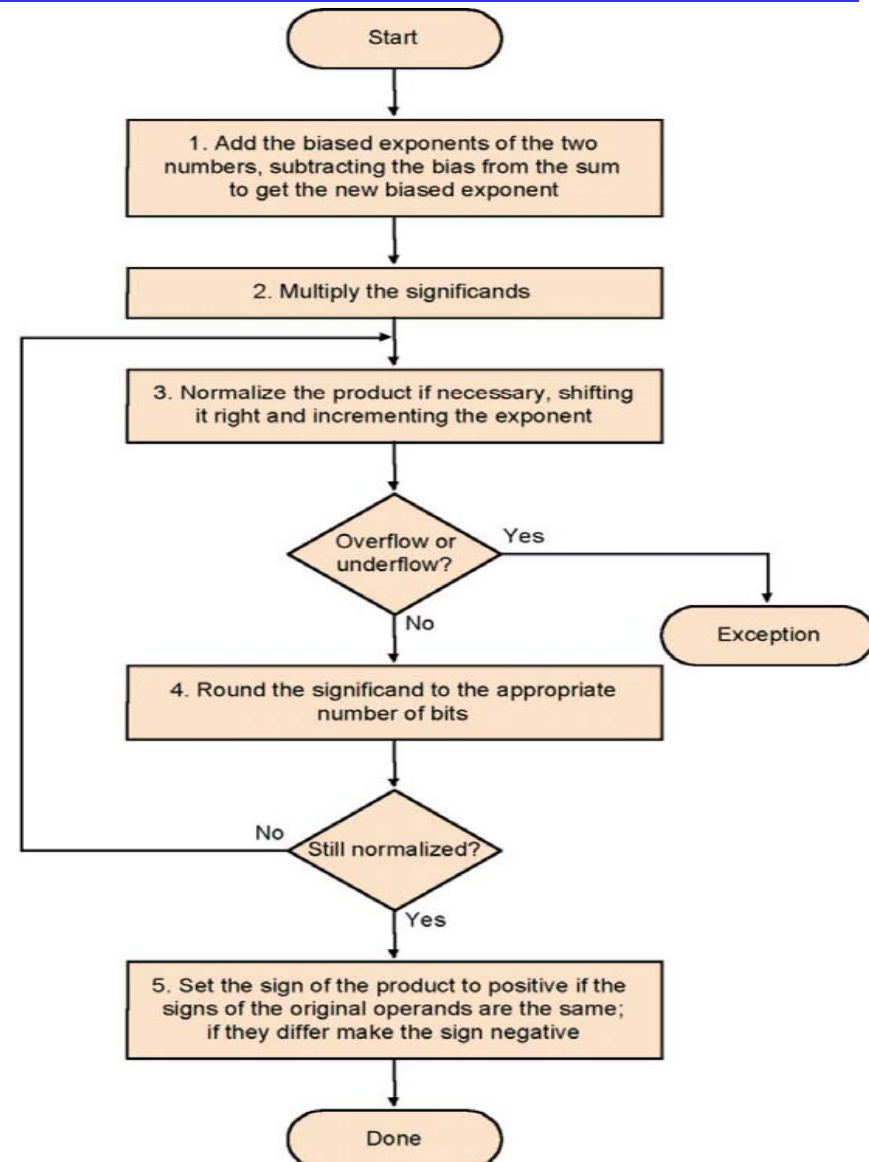- Add exponents
- Multiply the significands
- Normalize
- Over- underflow
- Rounding
- Sign




multiplying the numbers 0.5_{ten} and -0.4375_{ten}
 $\rightarrow 1.000_{\text{two}} \times 2^{-1}$ by $-1.110_{\text{two}} \times 2^{-2}$

- Step 1: Adding the exponents without bias or using the biased
 - $-1 + (-2) = -3$
 - $(-1 + 127) + (-2 + 127) - 127 = (-1 - 2) + (127 + 127 - 127)$
 $= -3 + 127 = 124$
- Step 2. Multiplying the significands
 - $1.110000_{\text{two}} \times 2^{-3}$
- Step 3. normalize
 - $127 \geq -3 \geq -126$, no overflow or underflow.
- Step 4. Rounding
 - $1.110_{\text{two}} \times 2^{-3}$
- Step 5. sign
 - $-1.110_{\text{two}} \times 2^{-3} = -0.21875_{\text{ten}}$

$$\begin{array}{r}
 1.000_{\text{two}} \\
 \times 1.110_{\text{two}} \\
 \hline
 0000 \\
 1000 \\
 1000 \\
 1000 \\
 \hline
 1110000_{\text{two}}
 \end{array}$$

FP Multiplier Hardware

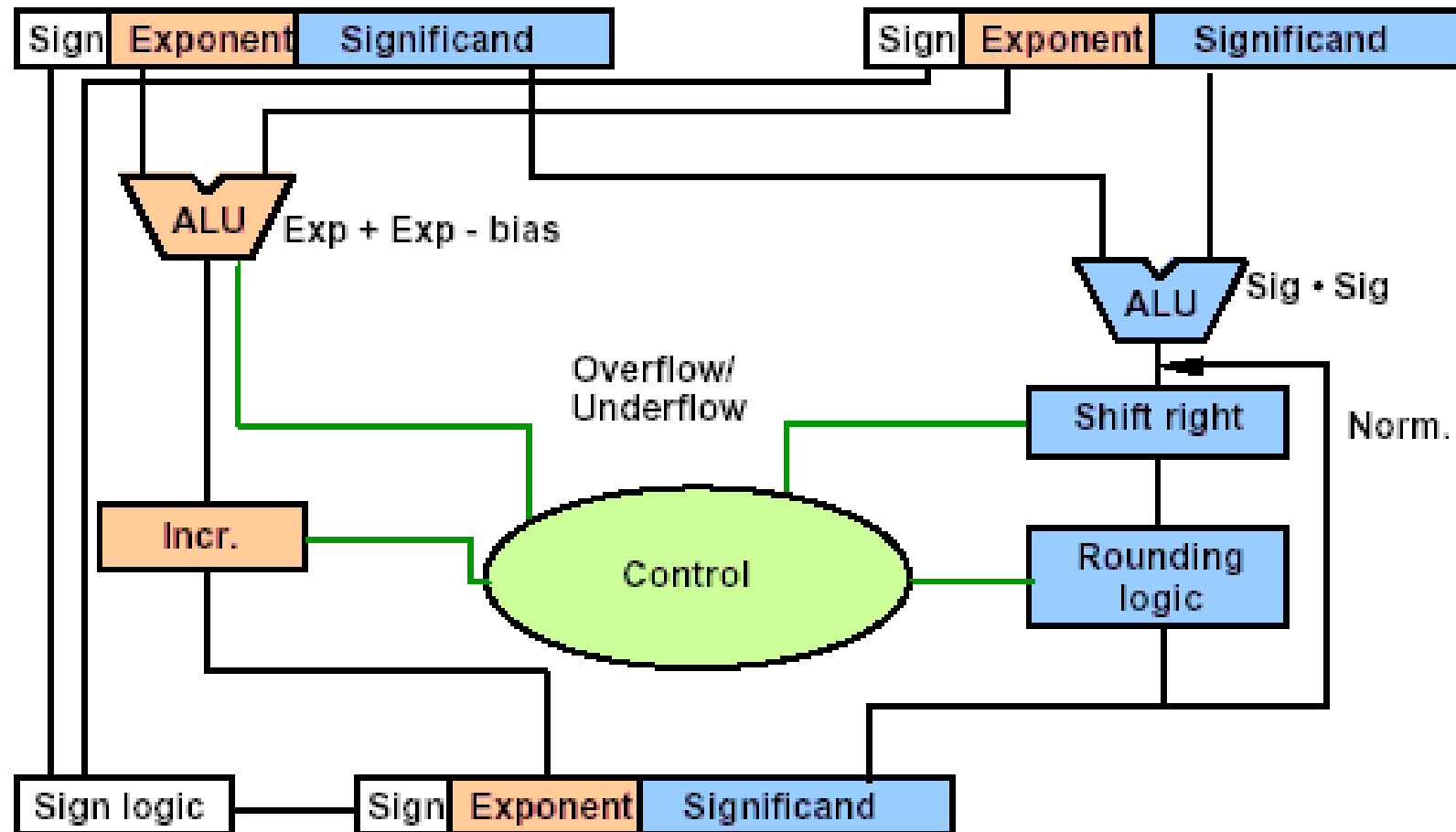

FP Arithmetic Hardware

- FP multiplier is of similar complexity to FP adder
 - But uses a multiplier for significands instead of an adder
- FP arithmetic hardware usually does
 - Addition, subtraction, multiplication, division, reciprocal, square-root
 - FP \leftrightarrow integer conversion
- Operations usually takes several cycles
 - Can be pipelined

Division-- Brief

- Subtraction of exponents
- Division of the significands
- Normalization
- Rounding
- Sign

Parallelism and Computer Arithmetic: Associativity

- $x + (y + z) = (x + y) + z$?
 - $x = -1.5_{\text{ten}} \times 10^{38}$, $y = 1.5_{\text{ten}} \times 10^{38}$,
and $z = 1.0$
 - $x + (y + z) = 0.0$
 - $(x + y) + z = 1.0$

END